

EE537 Circuit Simulation Lab

Experiment 6

Name: <PRIKSHAT SHARMA>

ID Number: <2023EEM1023>

September 27, 2024

Aim: Design and characterization of differential amplifier.

1 DIFFERENTIAL AMPLIFIER

A differential amplifier with NMOS input transistors and resistive load is shown in Fig. 1. $I_{REF} = 10 \mu A$, $V_{in,cm} = 900 mV$, $(W/L)M1 = (W/L)M2 = 20 \mu/1\mu$, $(W/L)M3 = (W/L)M4 = 2 \mu/1\mu$, $R_D = 100 K\Omega$. Derive the expressions for: 1) the small signal differential voltage gain($A_{v,dm}$), 2) the small signal common-mode voltage gain($A_{v,cm,cm}$)

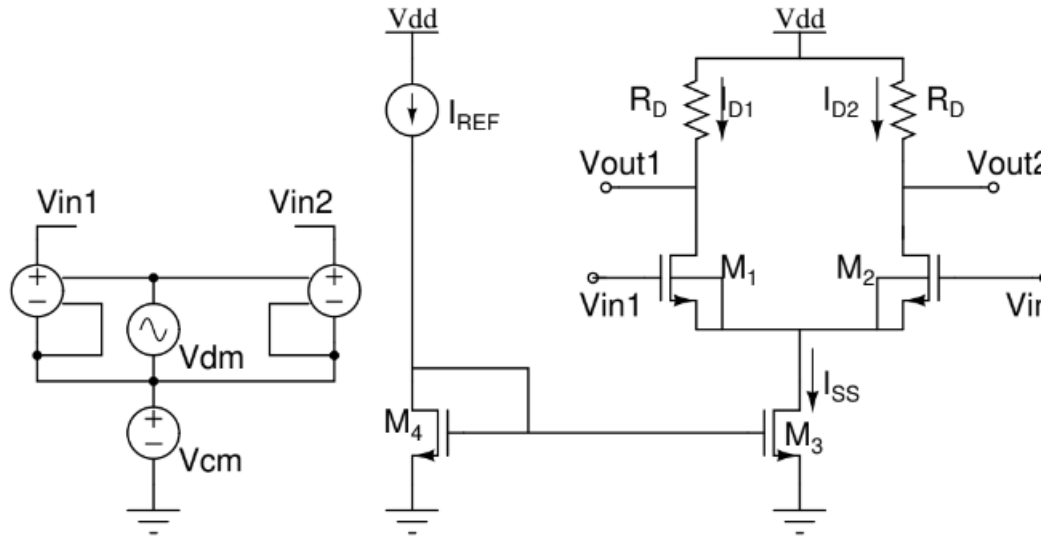


Figure 1: Differential amplifier with NMOS input transistors

Small signal differential gain($A_{v_{dm}}$),
Using Thevenin's equivalent method.
So, we have to find

$$\frac{V_x}{V_{in1}}$$

with V_{in2} tends to 0(1)

$$\frac{V_y}{V_{in1}}$$

with V_{in2} tends to 0(2)

Now we can say

$$V_x - V_y = f(V_{in1})$$

$$\text{Similarly } V_x - V_y = f(v_{in2})$$

to find the $A_{v_{dm}}$

$$A_{v_{dm}} = \frac{V_x - V_y}{V_{in1} - V_{in2}} \quad (3)$$

Considering matched transistors

$$\frac{V_x}{V_{in1}}$$

with $V_{in2} = 0$ (4)

$$\frac{V_x}{V_{in1}} = \frac{-RD1}{\frac{1}{g_m} + RS} = \frac{-RD1}{\frac{1}{gm1} + \frac{1}{gm2}} \quad (5)$$

$$\frac{V_{in1}}{\frac{1}{gm1} + \frac{1}{gm2}} = \frac{V_y}{RD1} \quad (6)$$

from 5 and 6

$$\frac{V_x - V_y}{V_{in1}} = \frac{-2RD1}{\frac{1}{gm1} + \frac{1}{gm2}} \quad (7)$$

Assuming $gm1 = gm2 = gm$ and $RD1 = RD2 = RD$

$$\frac{V_x - V_y}{V_{in1}} = -gm * RD \quad (8)$$

Similarly;

$$\begin{aligned} V_x - V_y &= gm * R_D * V_{in2} \\ V_x - V_y &= -gm * R_D * V_{in1} + gm * R_D * V_{in2} \\ V_x - V_y &= -gm * R_D (V_{in1} - V_{in2}) \end{aligned}$$

Using superposition

$$A_{vdm} = \frac{V_x - V_y}{V_{in1} - V_{in2}} = -gm * R_D \quad (9)$$

Small signal common-mode voltage gain $A_{v,cm,cm}$

Again assuming that the circuit is symmetric, and the current source has finite output impedance. let it be R_{ss} $R_{d1} = R_{d2} = R_d$ and transistors are matched. the common mode gain is given by

$$A_{vcm} = \frac{V_{out}}{V_{in,cm}} \quad (10)$$

$$V_{gs} = V_{in,cm} - V_s \quad (11)$$

$$V_s = 2gm(V_{in,cm} - V_s)R_{ss} \quad (12)$$

$$V_s = \frac{2gmR_{ss}}{1 + 2gmR_{ss}} * V_{in,cm} \quad (13)$$

Kcl at Output terminal and using intuition

$$\frac{V_{out}}{\frac{R_d}{2}} + 2gm(V_{in,cm} - V_s) = 0 \quad (14)$$

$$\frac{V_{out}}{\frac{R_d}{2}} = -2gm(V_{in,cm} - V_s) \quad (15)$$

$$\frac{V_{out}}{\frac{R_d}{2}} = -2gm(V_{in,cm} - \frac{2gmR_{ss}V_{in,cm}}{1 + 2gmR_{ss}}) \quad (16)$$

or

$$\frac{V_{out}}{V_{in,cm}} = \frac{-gmR_d}{1 + 2gmR_{ss}} \quad (17)$$

- 2 Plot V_{out1} , V_{out2} , V_p , $ID1$, $ID2$ vs common mode input voltage. Sweep the common mode input voltage from 0 to V_{dd} .

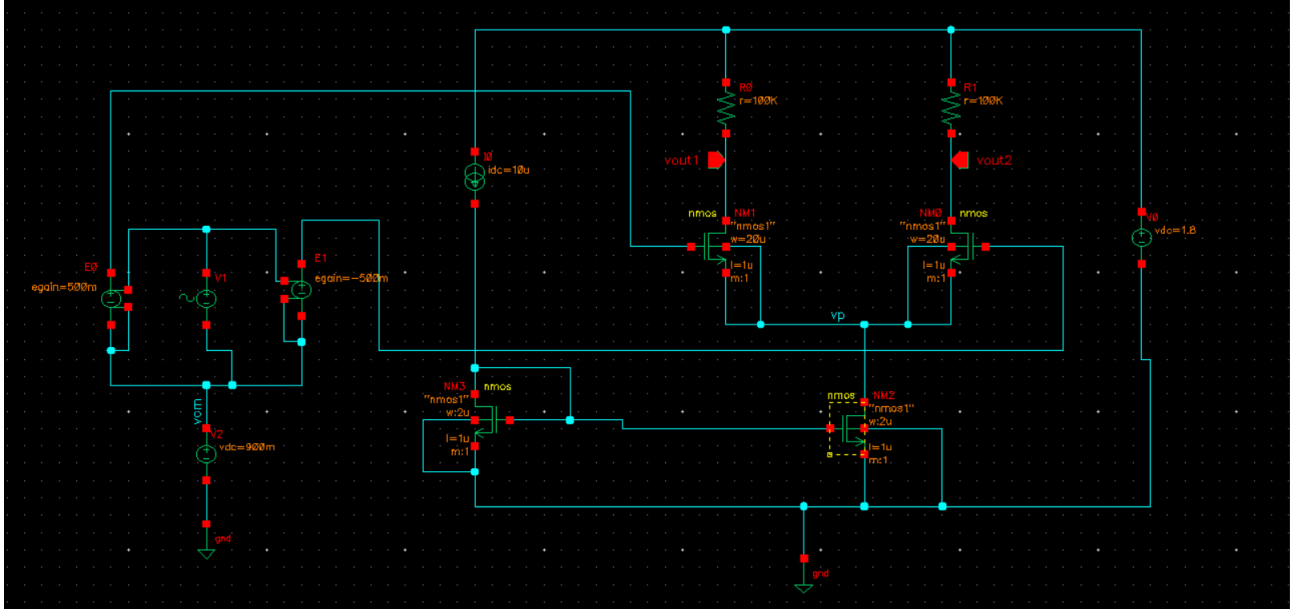


Figure 2: Ckt diagram for plotting the above variables

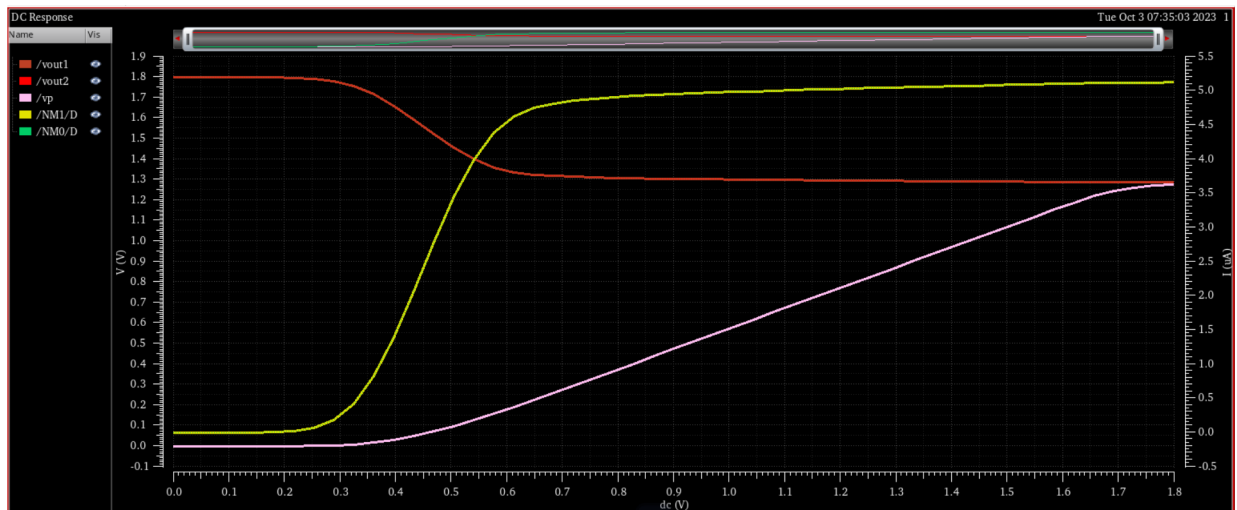


Figure 3: V_{out1} , V_{out2} , V_p , I_{out1} , I_{out2} wrt V_{cm}

- Plot V_{out1} , V_{out2} , $V_{out2} - V_{out1}$, V_p , I_{D1} , I_{D2} vs differential input voltage for a common mode input voltage of 0.9 V. Sweep the differential input voltage from -400mV to 400mV.

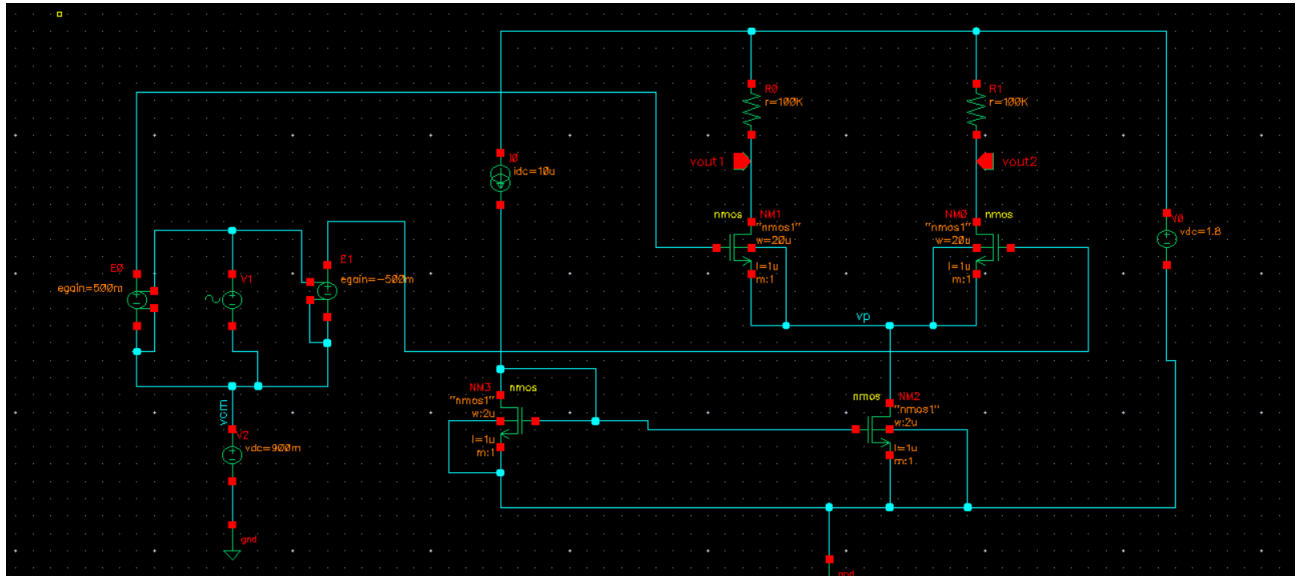


Figure 4: Ckt diagram for plotting the above variables

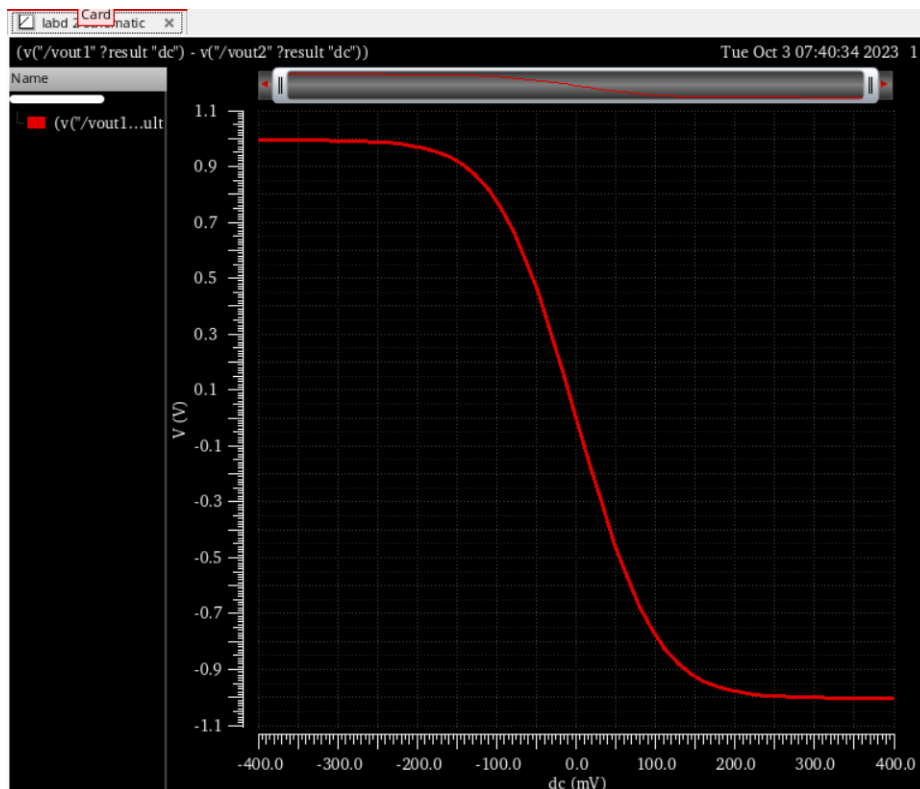


Figure 5: $V_{out2}-V_{out1}$ wrt V_{dm}

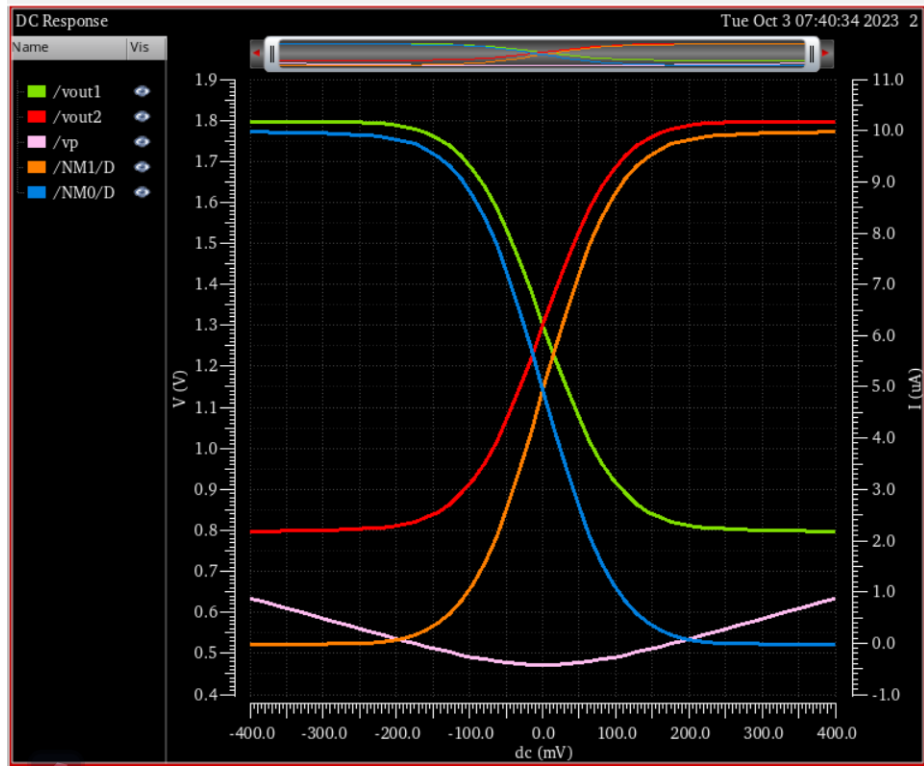


Figure 6: Vout1, Vout2, Vp, Iout1, Iout2 wrt Vdm

- 4 Plot differential mode gain($A_{v, dm}$) with common mode input voltage sweep from 0 to V_{dd} . What is the observed input common mode range(ICMR)?

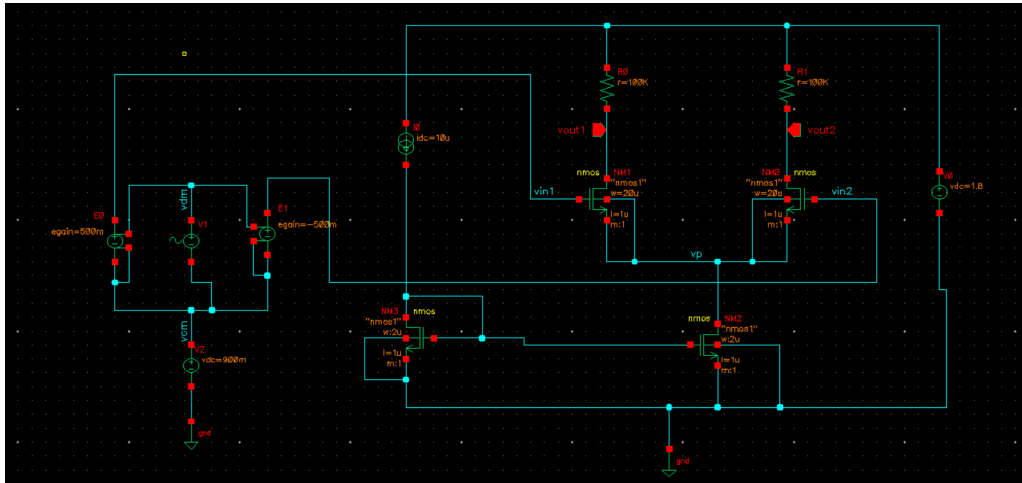


Figure 7: ckt diagram Differential mode gain wrt Vcm

The calculation for ICMR We know that

$$V_{gs1} + (V_{gs3} - V_{th3}) < V_{in, cm} < \min([V_{dd} - \frac{R_d I_d}{2} + V_{th}], V_{dd}) \quad (18)$$

So ICMR is

$$580mV < V_{in, cm} < 1.8V \quad (19)$$

Hence the range is 1220mV. The observed value of ICMR is $1.536V - 597.197mV = 939mV$

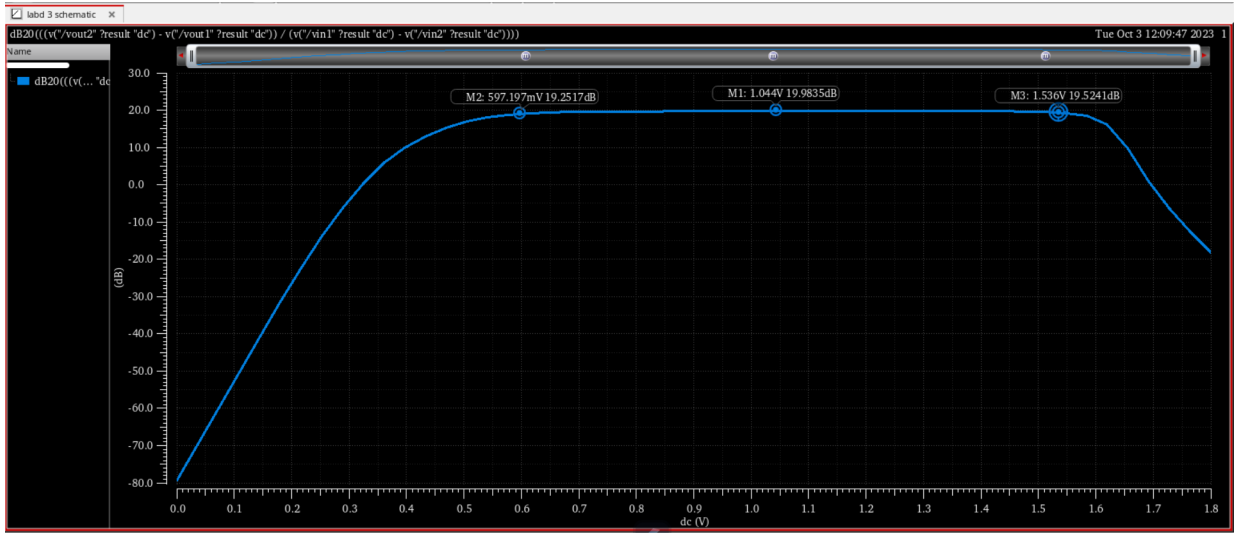


Figure 8: Differential mode gain wrt V_{cm}

- 5 Plot the differential mode gain ($A_{v,dm}$), common mode to differential mode gain ($A_{v,cmdm}$), common mode to common mode gain ($A_{v,cmcm}$) vs. frequency. Verify the low frequency values from calculations and simulations.

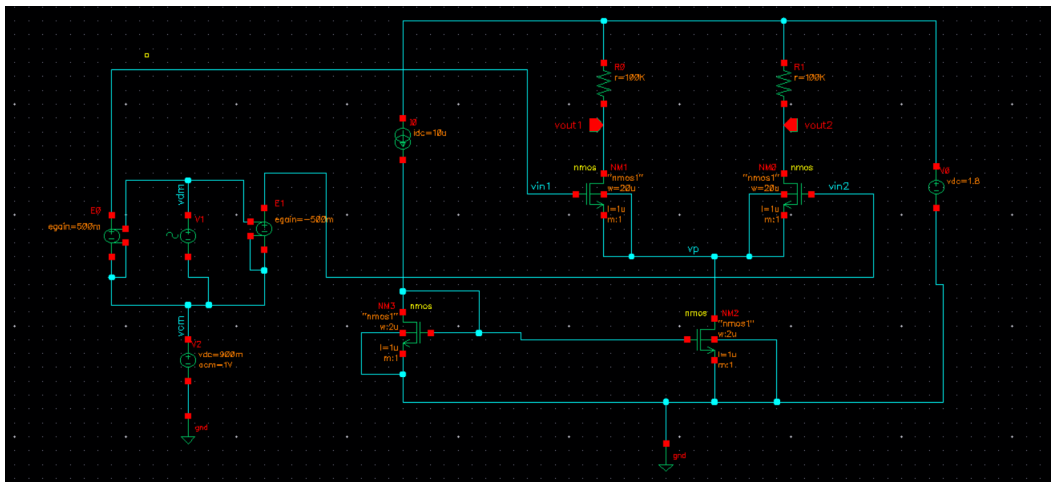


Figure 9: Ckt diagram Differential mode gain

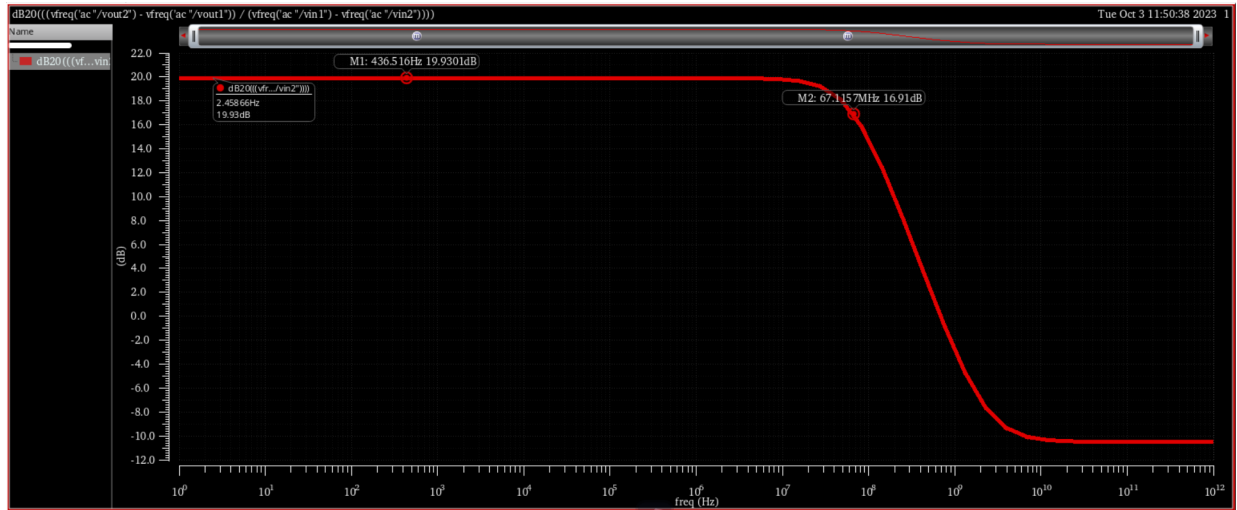


Figure 10: Differential mode gain wrt freq

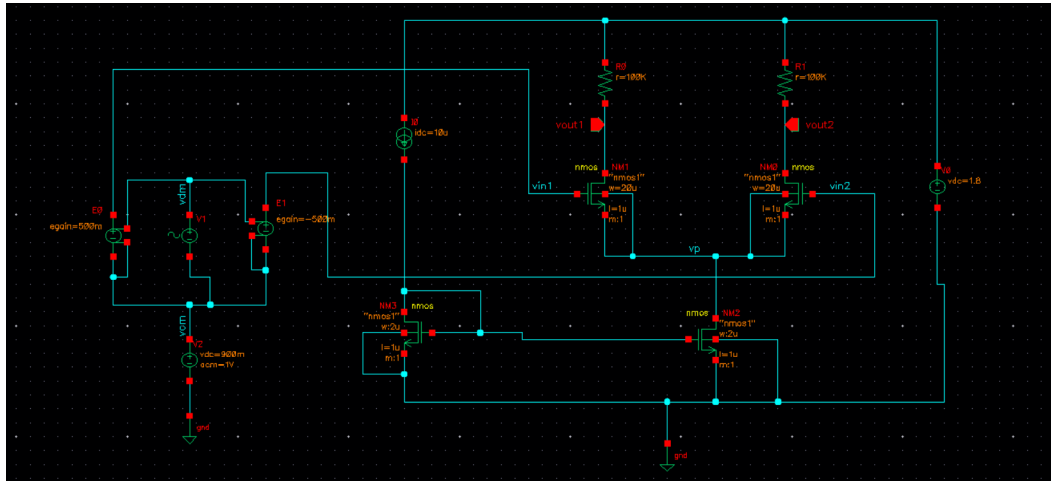


Figure 11: ckt diagram common mode to differential mode gain

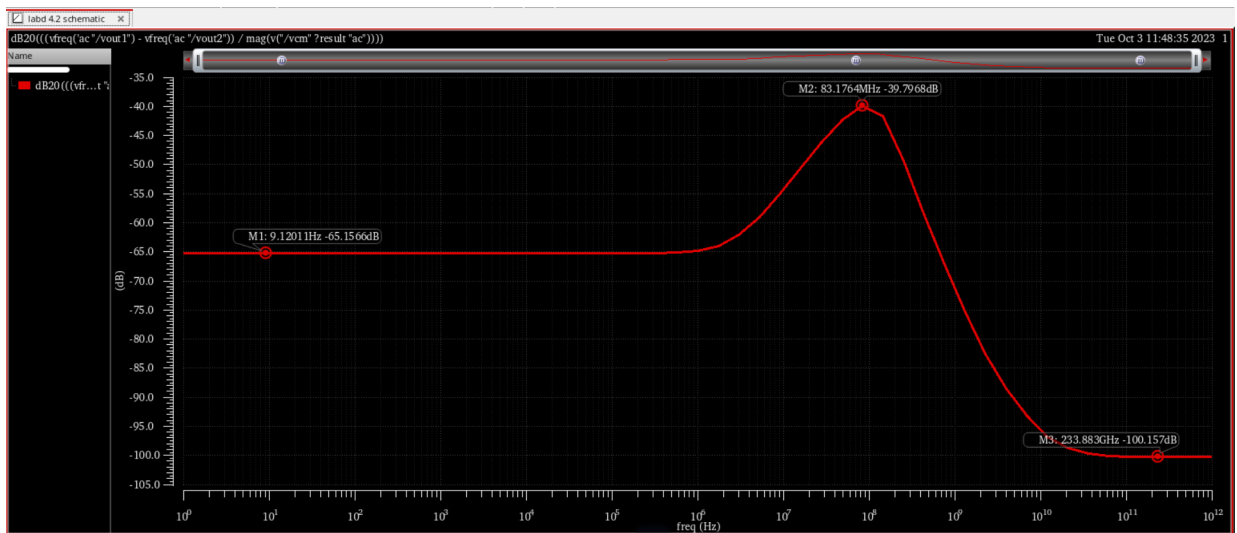


Figure 12: common mode to differential mode gain wrt freq

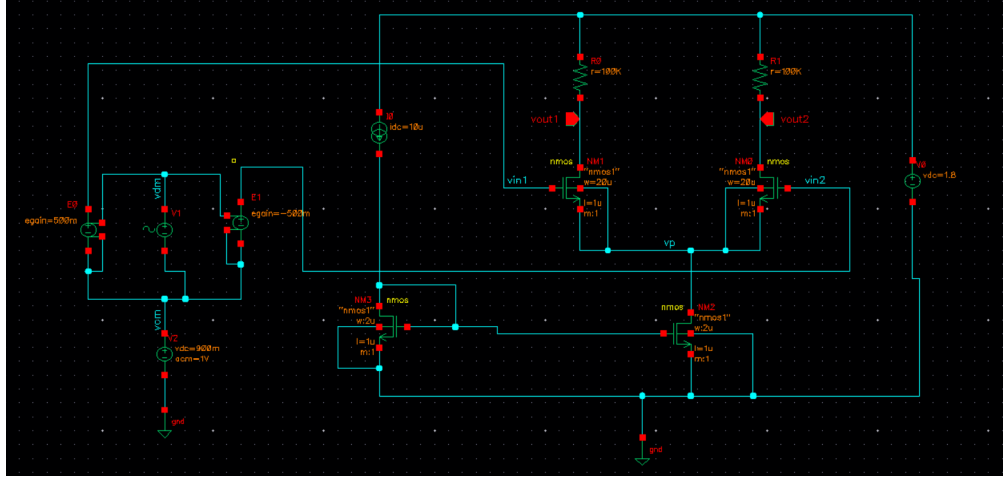


Figure 13: Ckt diagram for common mode to common mode gain

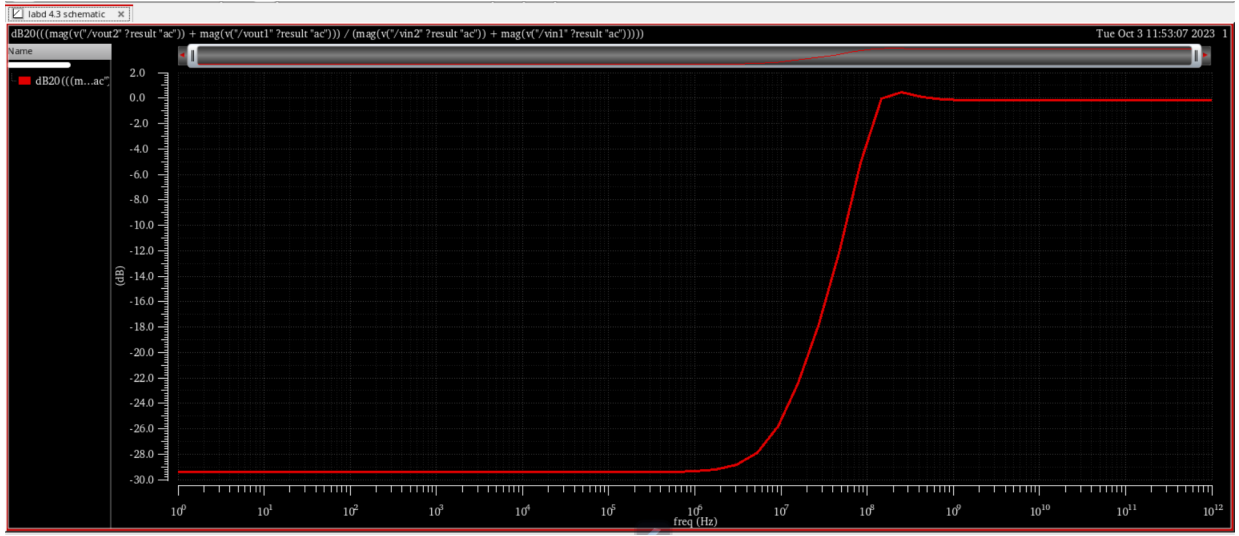


Figure 14: common mode to common mode gain wrt freq

Hand Calculations

$$A_{v, dm} = -gmR_d \quad (20)$$

$$A_v = -104.09\mu \times 100k \quad (21)$$

$$A_v = -10.409 \quad (22)$$

In dB

$$|A_v|_{dB} = 20\log(|-10.409|) = 20.34dB \quad (23)$$

For $A_{v, cm, dm}$

$$A_{vcm, dm} = \frac{-dgmR_d}{(gm1 + gm2)R_{ss} + 1} \quad (24)$$

$$dgm = gm1 - gm2 = 104.09\mu - 102.21\mu = 2\mu A \quad (25)$$

$$gm1 + gm2 = 104.09 + 102.21 = 206.3\mu A \quad (26)$$

$$R_{ss} = r_{out3} = 1.457M\Omega \quad (27)$$

$$|A_{vcm, dm}| = \frac{2\mu \times 100k}{(206\mu \times 1.457M) + 1} \quad (28)$$

$$|A_{vcm, dm}|_{dB} = 20\log(|A_{vcm, dm}|) = -63.5dB \quad (29)$$

$$A_{vcm, cm} = \frac{\frac{-R_d}{2}}{\frac{1}{2g_m} + R_{ss}} \quad (30)$$

R_{ss} is resistance of the current source

$$|A_{vcm, cm}| = \frac{\frac{100k}{2}}{\frac{1}{2 \times 104u} + 1.457M} = .034 \quad (31)$$

$$|A_{vcm, cm}| = 20\log(0.034) = -29.31dB \quad (32)$$

- 6 Plot the differential mode gain($A_{v, dm}$), common mode to differential mode gain ($A_{v, cmdm}$), common mode to common mode gain ($A_{v, cm-cm}$) and CMRR vs. frequency with 10% mismatch in R_d .

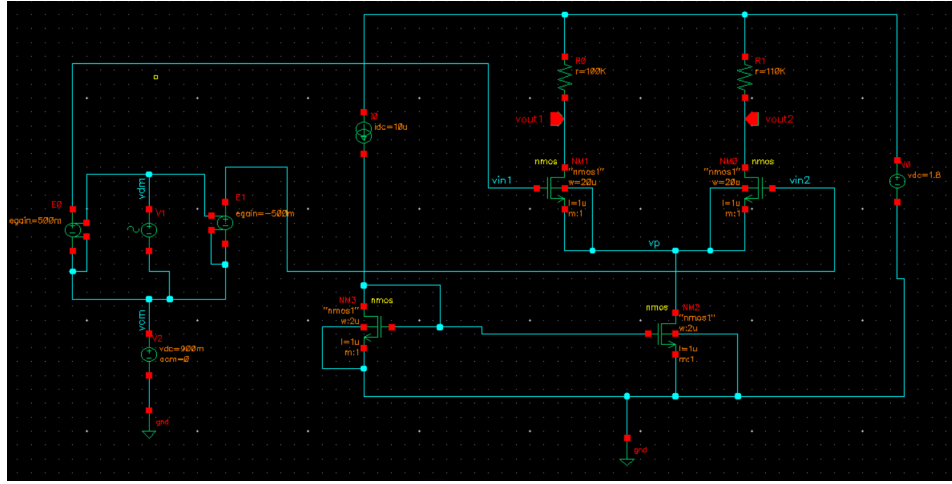


Figure 15: Differential mode gain wrt freq with 10% mismatch ckt diagram



Figure 16: Differential mode gain wrt freq with 10% mismatch vs freq

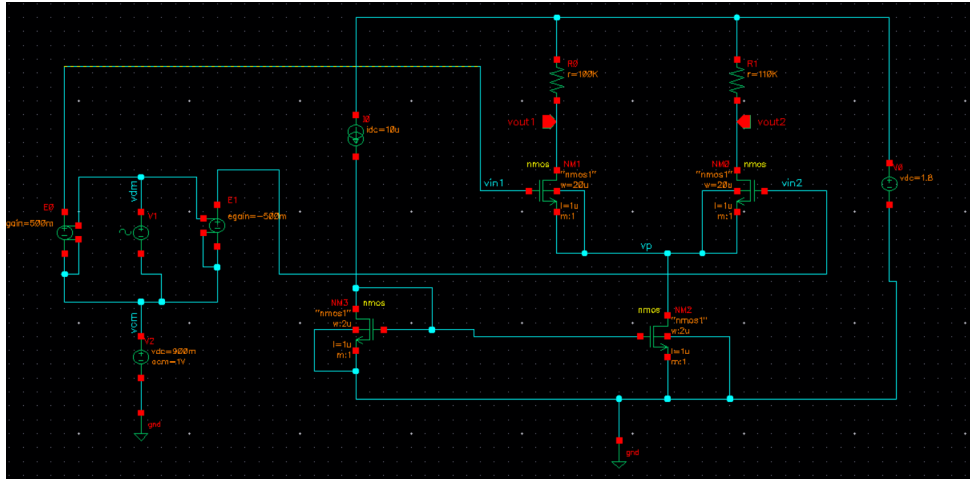


Figure 17: common mode to differential mode gain wrt freq with 10% mismatch ckt diagram

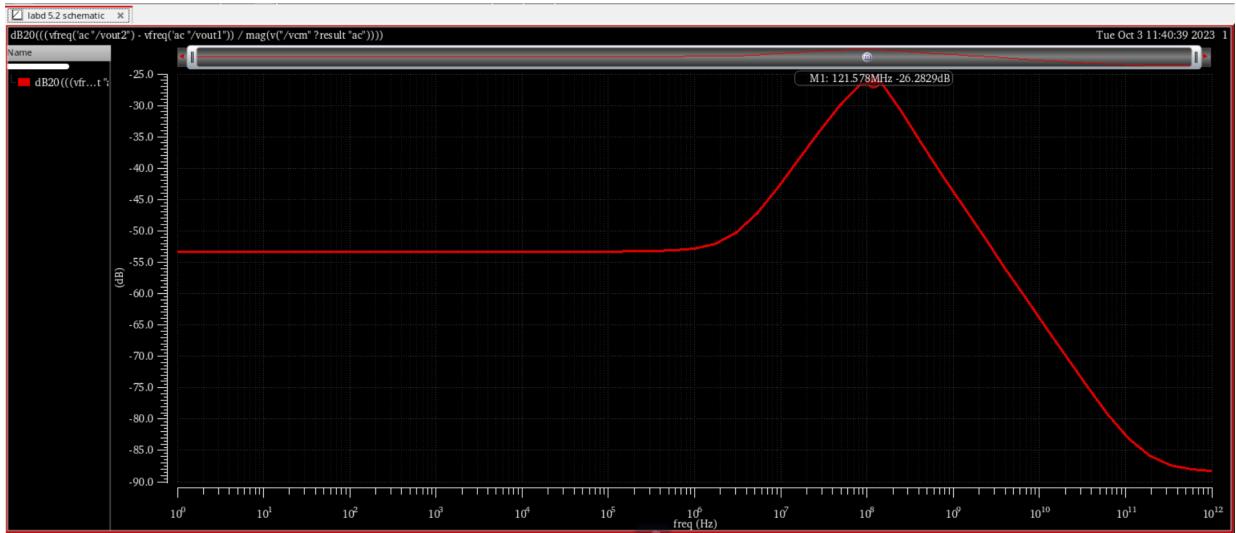


Figure 18: common mode to differential mode gain wrt freq with 10% mismatch vs freq

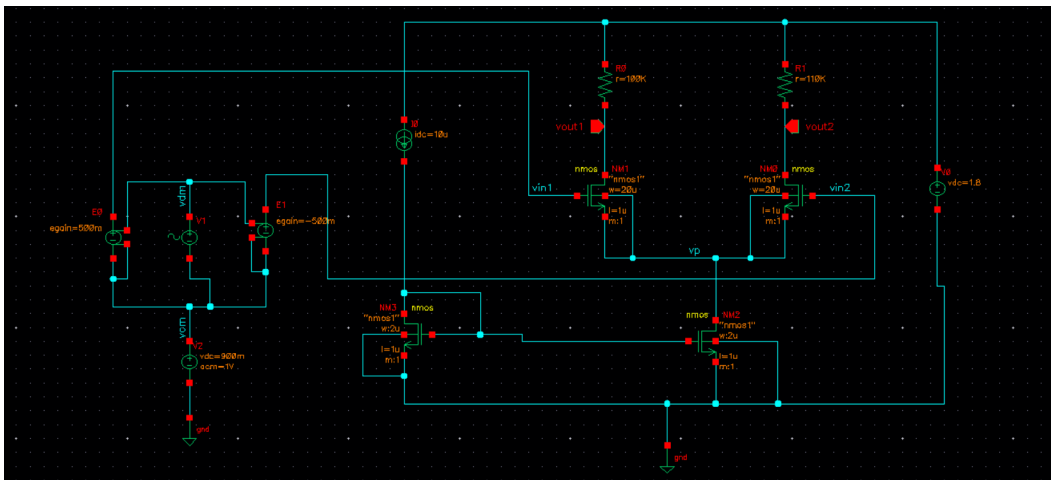


Figure 19: common mode to common mode gain wrt freq with 10% mismatch vs freq ckt diagram

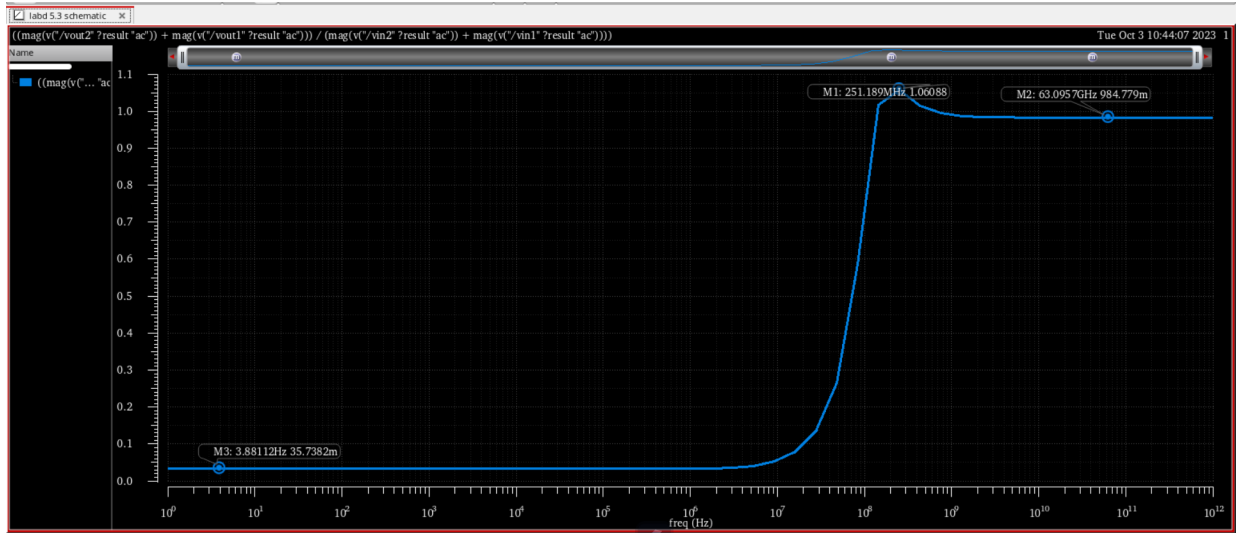


Figure 20: common mode to common mode gain wrt freq with 10% mismatch vs freq

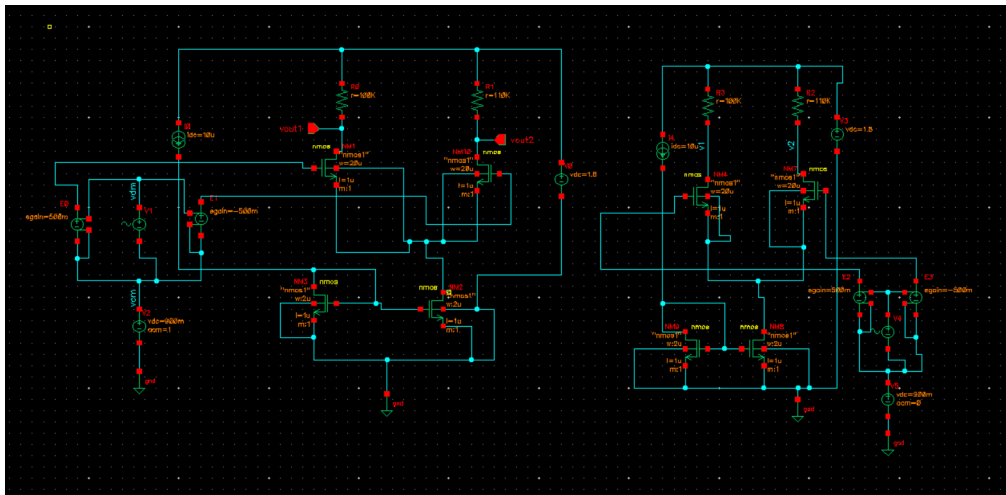


Figure 21: Ckt diagram to calculate the CMRR

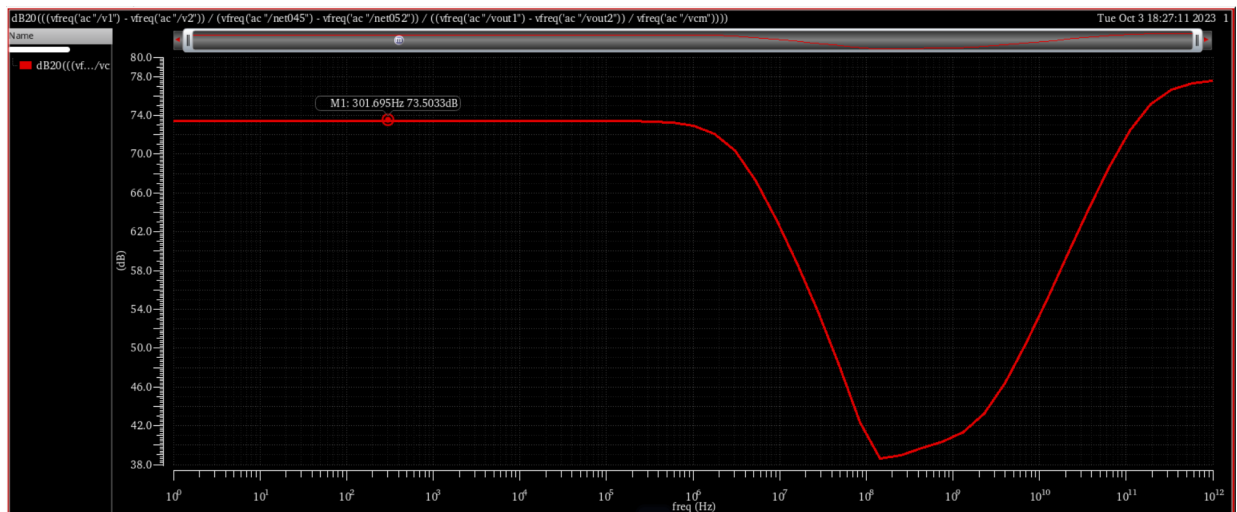


Figure 22: CMRR vs Frequency

- 7 Plot the power spectral density of input referred noise and output noise. Also present the integrated noise summary. The integration bandwidth is from 1 Hz to $\frac{\pi}{2}$ f_{3,db}.

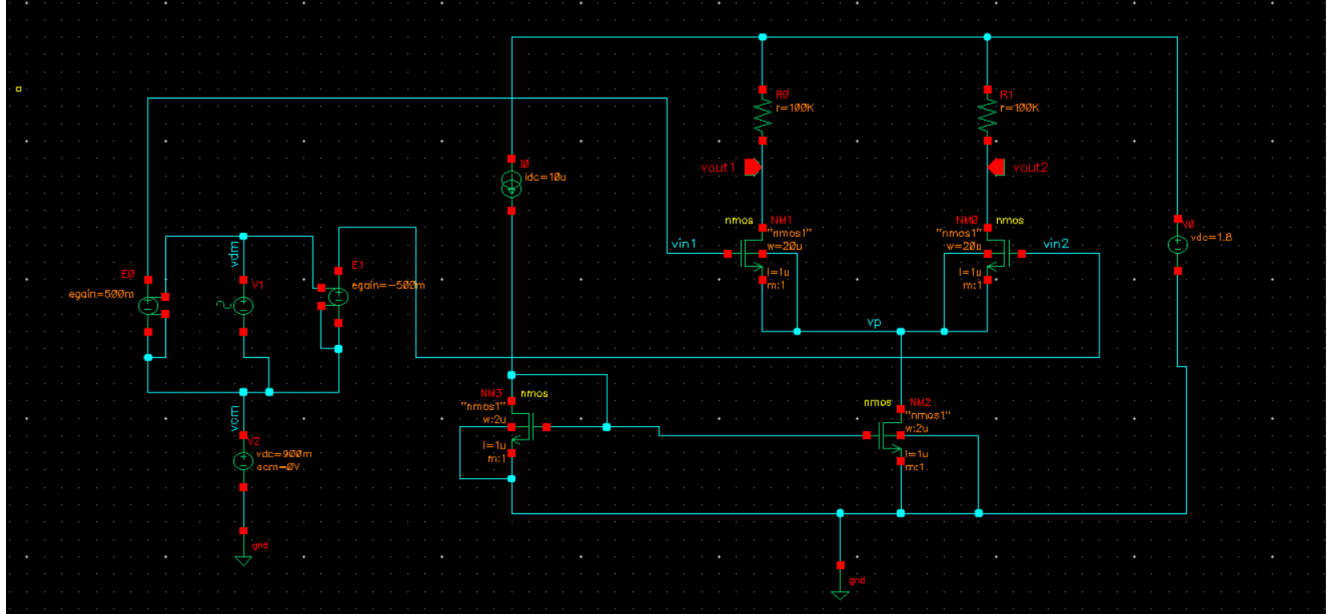


Figure 23: Ckt for plotting PSD

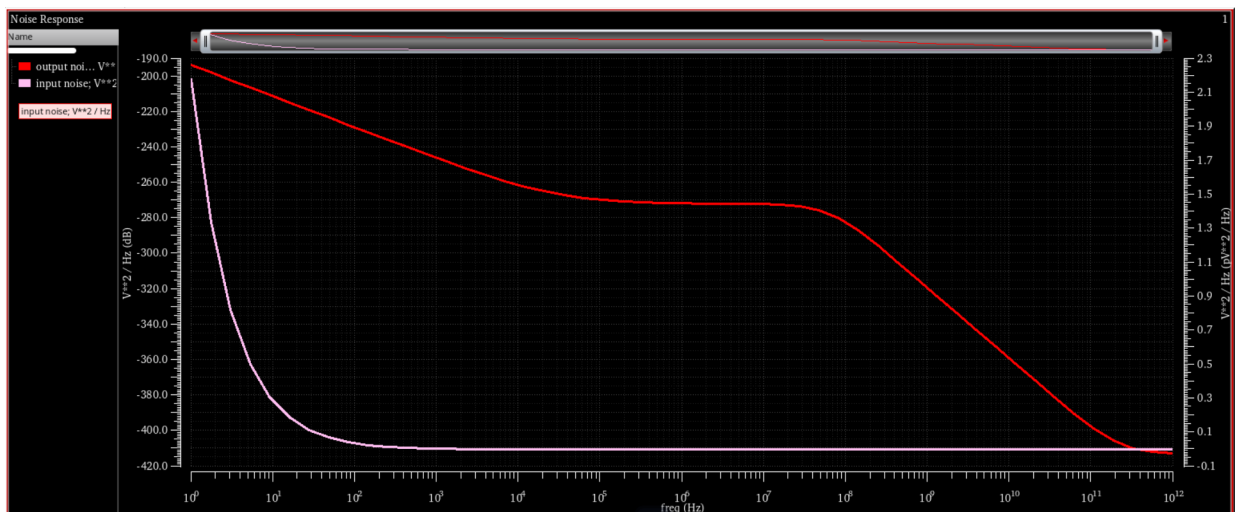


Figure 24: Power spectral density of input referred noise and output noise

Device	Param	Noise Contribution	% Of Total
/NM0	id	7.73733e-07	44.07
/NM1	id	7.59546e-07	43.27
/R0	rn	1.04638e-07	5.96
/R1	rn	1.03792e-07	5.91
/NM0	fn	6.75705e-09	0.38
Integrated Noise Summary (in V^2) Sorted By Noise Contributors			
Total Summarized Noise = 1.7555e-06			
Total Input Referred Noise = 2.7529e-08			
The above noise summary info is for noise data			
Device	Param	Noise Contribution	% Of Total
/NM0	id	7.73733e-07	44.07
/NM1	id	7.59546e-07	43.27
/R0	rn	1.04638e-07	5.96
/R1	rn	1.03792e-07	5.91
/NM0	fn	6.75705e-09	0.38
Integrated Noise Summary (in V^2) Sorted By Noise Contributors			
Total Summarized Noise = 1.7555e-06			
Total Input Referred Noise = 2.7529e-08			
The above noise summary info is for noise data			

Figure 25: Integration bandwidth is from 1 Hz to $\frac{\pi}{2} \cdot f_3$,db