

---

# EE537 Circuit Simulation Lab

## Experiment 6B

Name: <PRIKSHAT SHARMA>

ID Number: <2023EEM1023>

September 27, 2024

---

## 1 Design of differential amplifier with resistive load

Design a differential amplifier with resistive load, tail current source of  $23 \times (10) \mu A$ . The ICMR should be 1.2 V,  $f_{3db} < 1$  MHz and maximize the voltage gain and minimize the common mode gain. Use a load capacitor at the output to band limit the amplifier. Bias the tail current source by using the available reference current of  $I_{REF} = 10 \mu A$ .

### 1.1 Hand Calculations

Given tail current source to be  $23 \times (10) = 230 \mu A$

#### 1.1.1 Calculating W/L for Input transistors

Calculating the W/L values for the input transistors As we know that as per symmetry considerations  $I_1 + I_2 = 230 \mu A$   $I_1 = I_2$  hence  $I_1 = I_2 = 115 \mu A$  For the input transistors assuming the overdrive to be 100mV

$$I_d = \frac{\mu C_{ox} W (V_{gs} - V_t)^2}{2L} \quad (1)$$

putting the values we get,

$$115 \mu = 300 \mu * 0.01 * W/L * 0.5 \quad (2)$$

or  $W/L = 76.66$  Similar value will be taken for input transistor 2.

#### 1.1.2 Calculating the W/L for M3 and M4

Now for the tail current source the value of the W/L is given from (1) as

$$230 \mu = 300 \mu * 0.01 * W/L * 0.5 \quad (3)$$

From these we get  $W/L = 153.32$  Also the reference current source is given to be  $10 \mu A$ . The current will be mirrored from the reference current source. For this we can say, The ratios of W/L of the transistors 3 and 4 should be 23 to get the tail current source as  $230 \mu A$ .

#### 1.1.3 Calculating $V_{in,cm}$

The value of  $V_{in,cm}$ ; Given that  $ICMR = 1200mV$   $I_{cmr}$  is given by

$$V_{dd} - I_d R_s + V_{th1} - V_{gs1} - V_{ov3} = ICMR \quad (4)$$

$V_{ov3} = 100mV$ ,  $V_{gs1} - V_{th1} = 100mV$ ,  $V_{th1} = 500mV$ , so  $V_{gs1} = 600mV$ ,  $V_{in,cm} = V_{gs1} + V_{ov3}$ , or  $V_{in,cm} = 600mV + 100mV = 700mV$ .

### 1.1.4 Calculating Rd

Calculating the value of Rd; The maximum value that the ICMR can take is 1.8V so equating this to the  $V_{dd} - I_d R_s + V_{th}$  we can get Rd value i.e.  $1.8 - 115\mu R_d + 0.5 = 1.8$  or  $R_d = 4.34k\Omega$  Calculation of Capacitance  $f_{3dB} < 1MHz$

$$\frac{1}{2\pi RC} < 1M \quad (5)$$

$R=4.34\text{k}\Omega$  Hence putting the values we get

$$C > 37pF \quad (6)$$

Calculating the swing the maximum theoretical swing that is possible is  $V_{dd}-V_{in,cm}+V_{th}$  which is equal to 1.5V

Hence the amplitude value is taken to be 100mV

1.2 Show the plots verifying obtained swing, ICMR, differential gain and common mode gain.

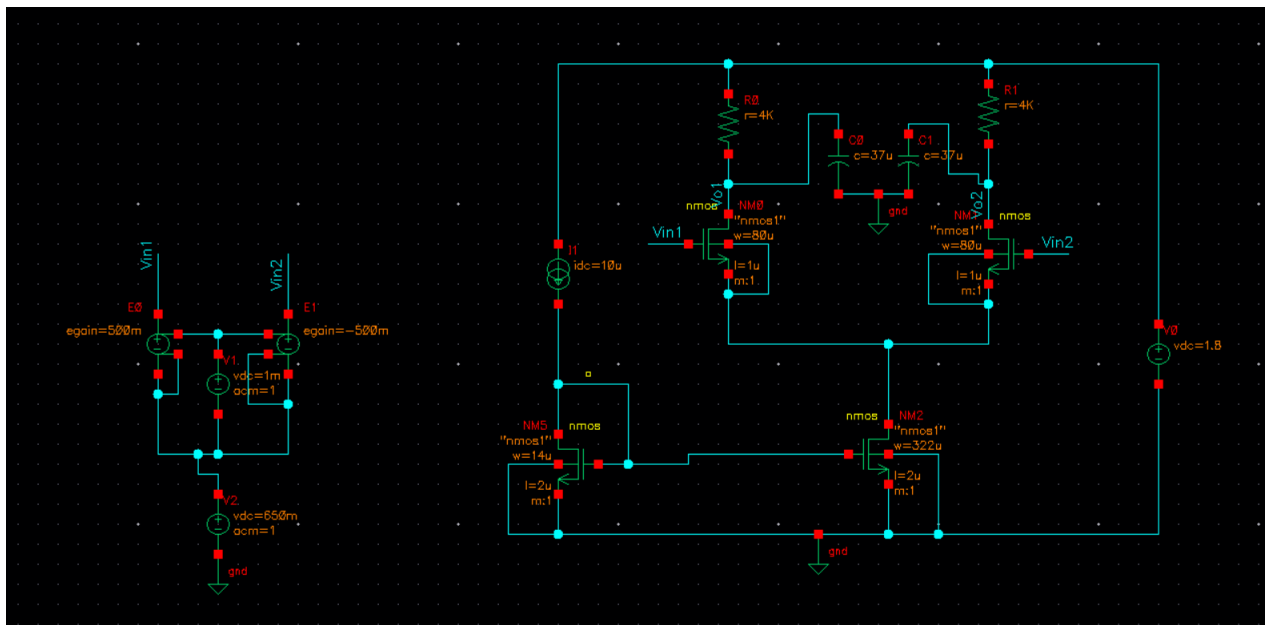


Figure 1: Ckt diagram for icmr calculation

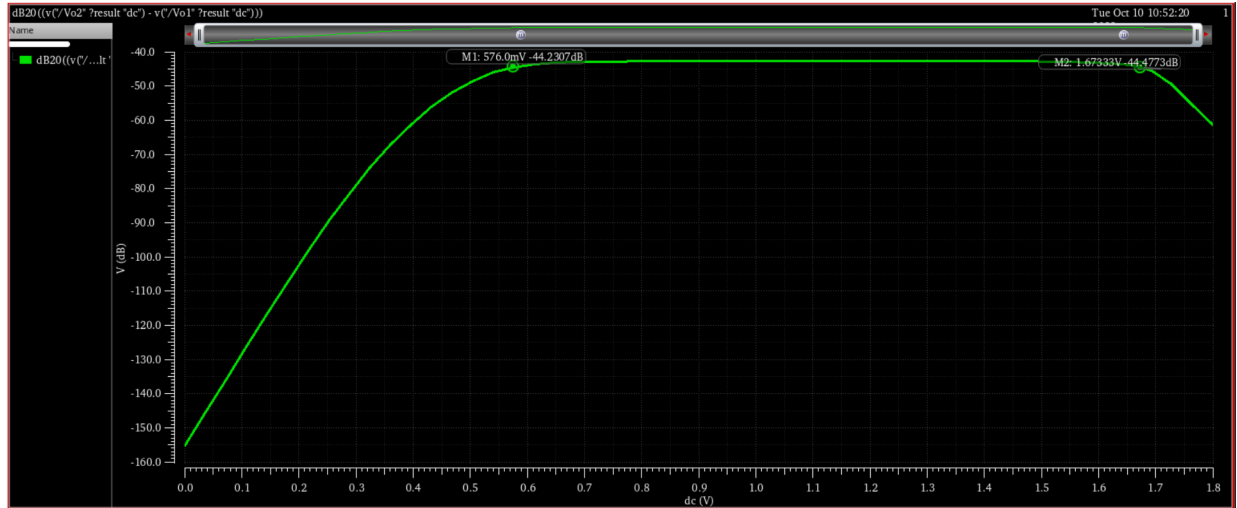


Figure 2: Plot of ICMR

The ICMR can be calculated as  $\min(V_{dd} - I_d R_s + V_{th}, V_{dd}) - V_{in,cm}$  which is given as  $V_{dd} - V_{in,cm}$  as,  $V_{dd} < V_{dd} - I_d R_s + V_{th}$ . Hence the value of ICMR is 1150mV. The Observed value is 1094mV

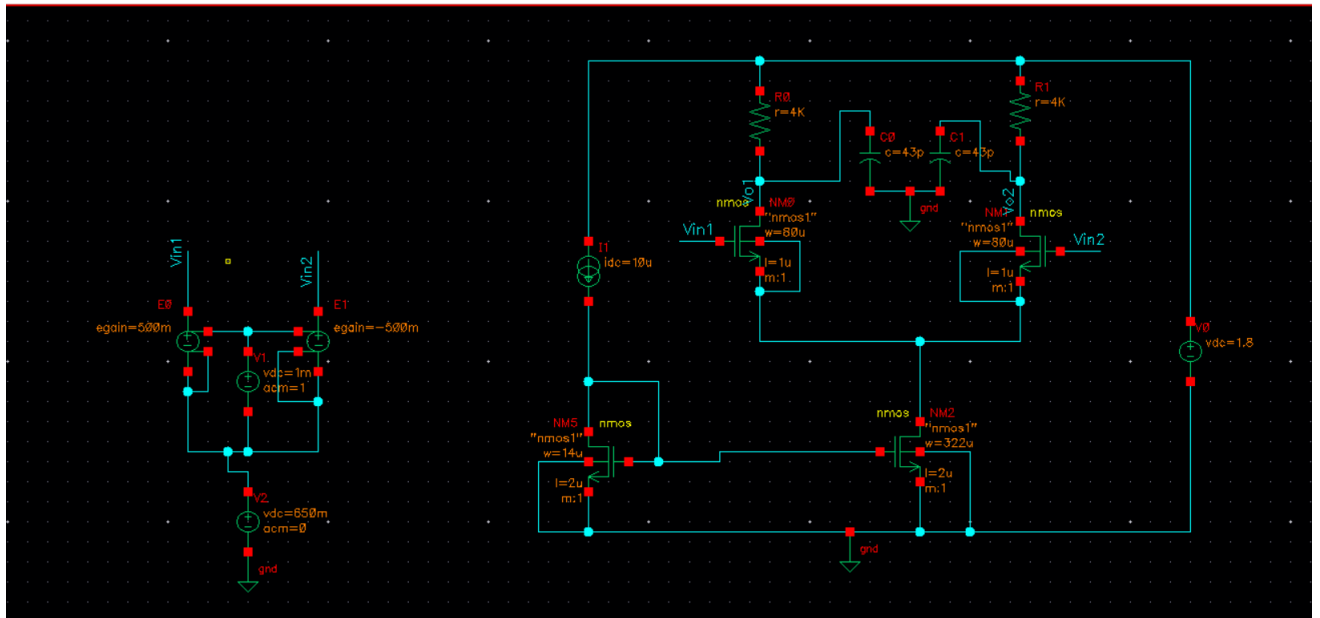


Figure 3: Ckt diagram for differential gain

The  $A_{vdm}$  is given by  $-g_m R_d$   
 $A_{vdm} = -g_m R_d = -1.85m \cdot 4k$

$A_{vdm} = -7.4$  which is approximately equal to 17dB.

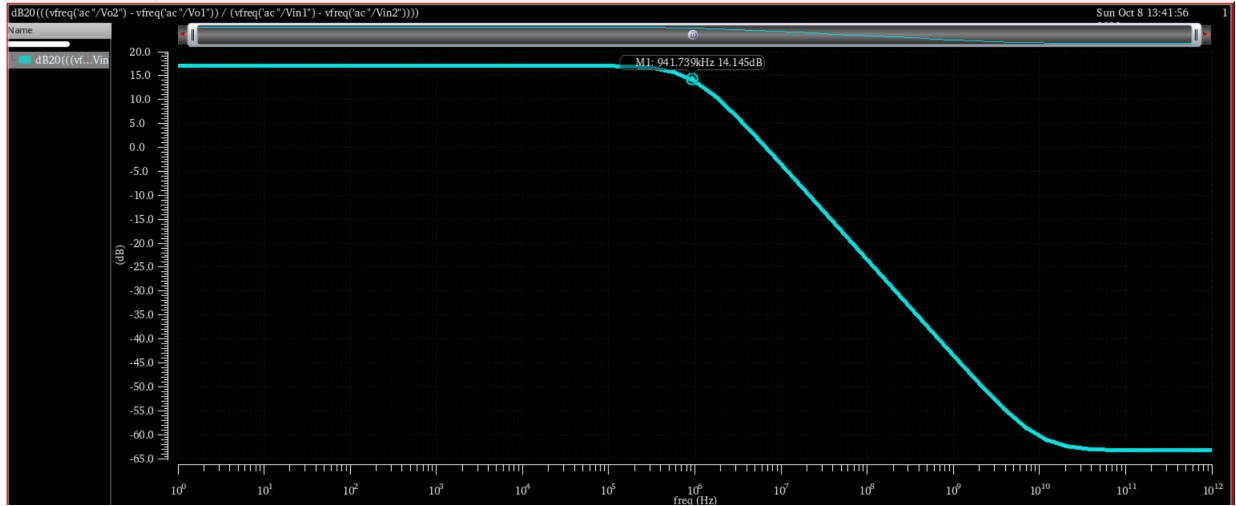


Figure 4: Differential gain wrt frequency

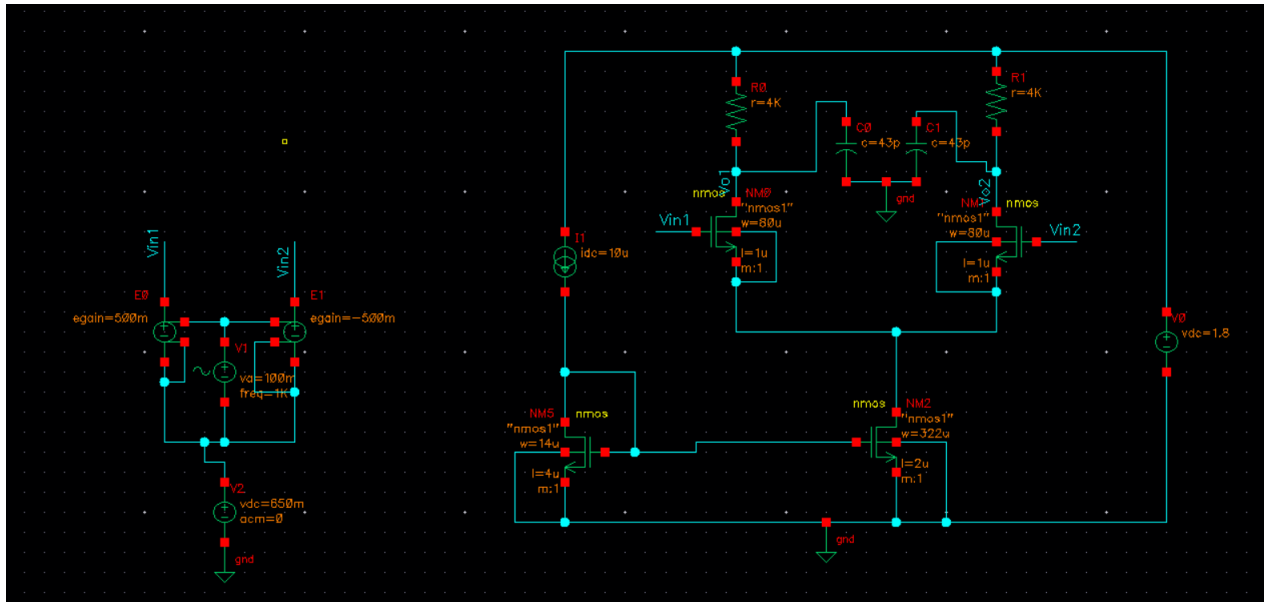


Figure 5: Ckt diagram for swing calculation

The swing can be given as  $\text{gain} \times \text{amplitude}$

The amplitude given is 100mV and the gain calculated is -7.4 the swing comes out to be 740mV and the observed swing is 850mV.

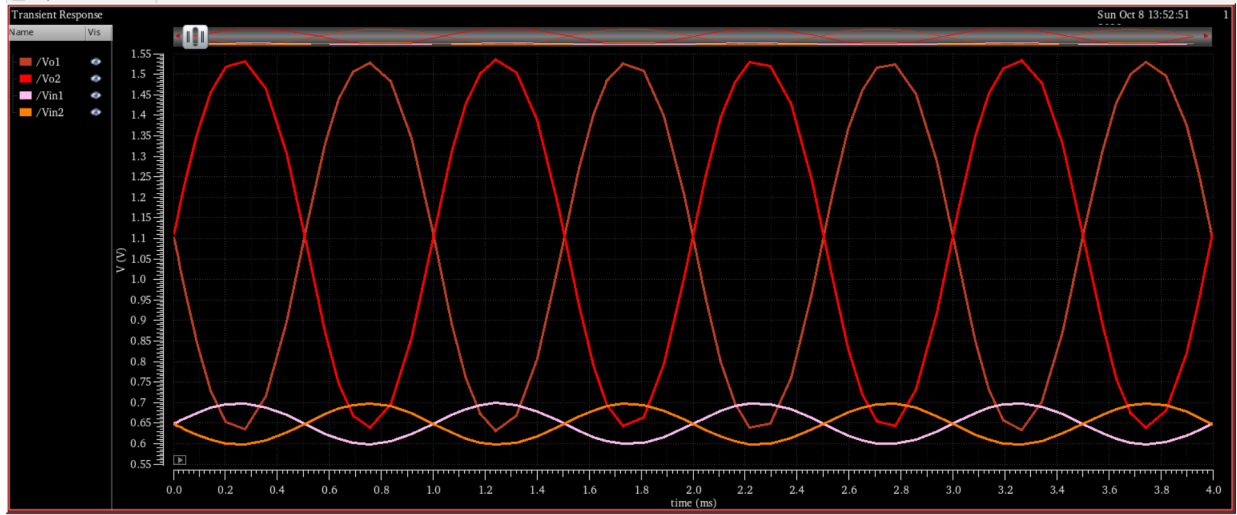


Figure 6: Swings wrt time

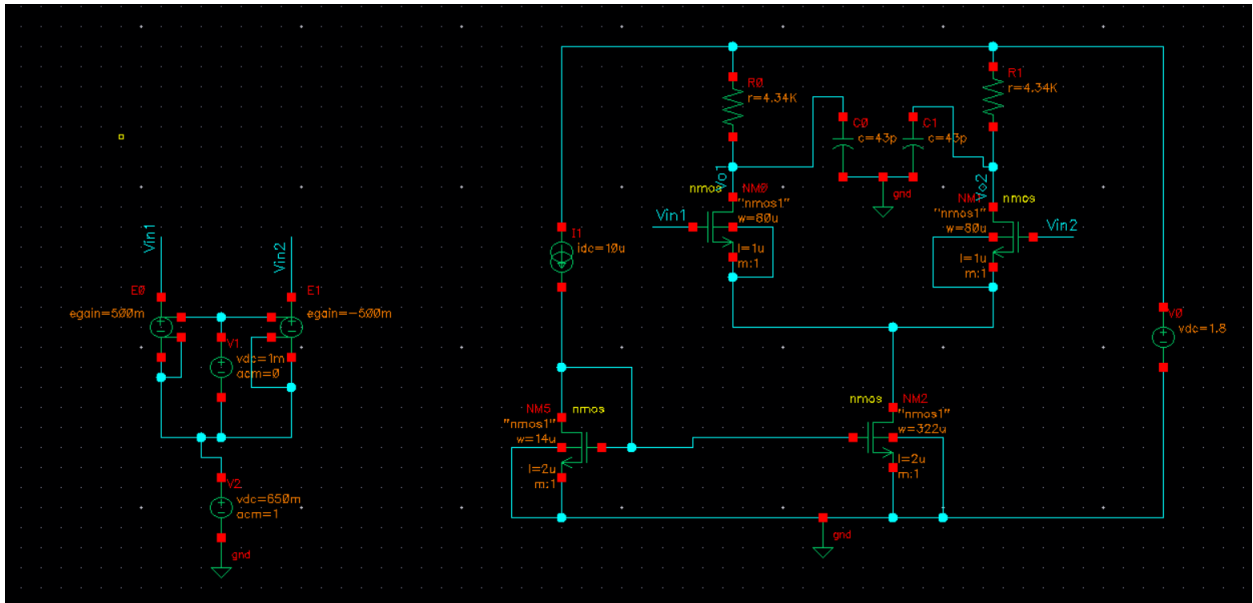


Figure 7: Ckt diagram for common mode gain


The common mode gain is given by

$$A_{vcm} = \frac{\frac{-R_d}{2}}{\frac{1}{2g_m} + R_{ss}} \quad (7)$$

$$A_{vcm} = \frac{\frac{-4.34k}{2}}{\frac{1}{2 \times 1.85m} + 4.1k} \quad (8)$$

$$A_{vcm} = 0.49 \quad (9)$$

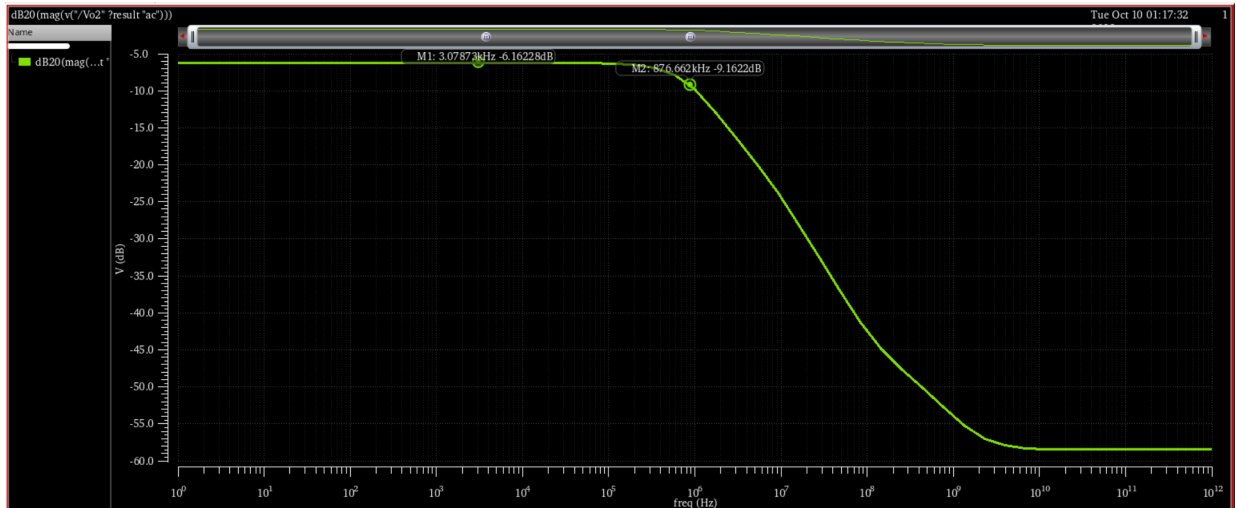The value of  $A_{vcm}$  in dB is around -6dB.



1.3 Compare the PSD of input referred noise with the PSD of noise observed in previous question. What is the effect of power on PSD?

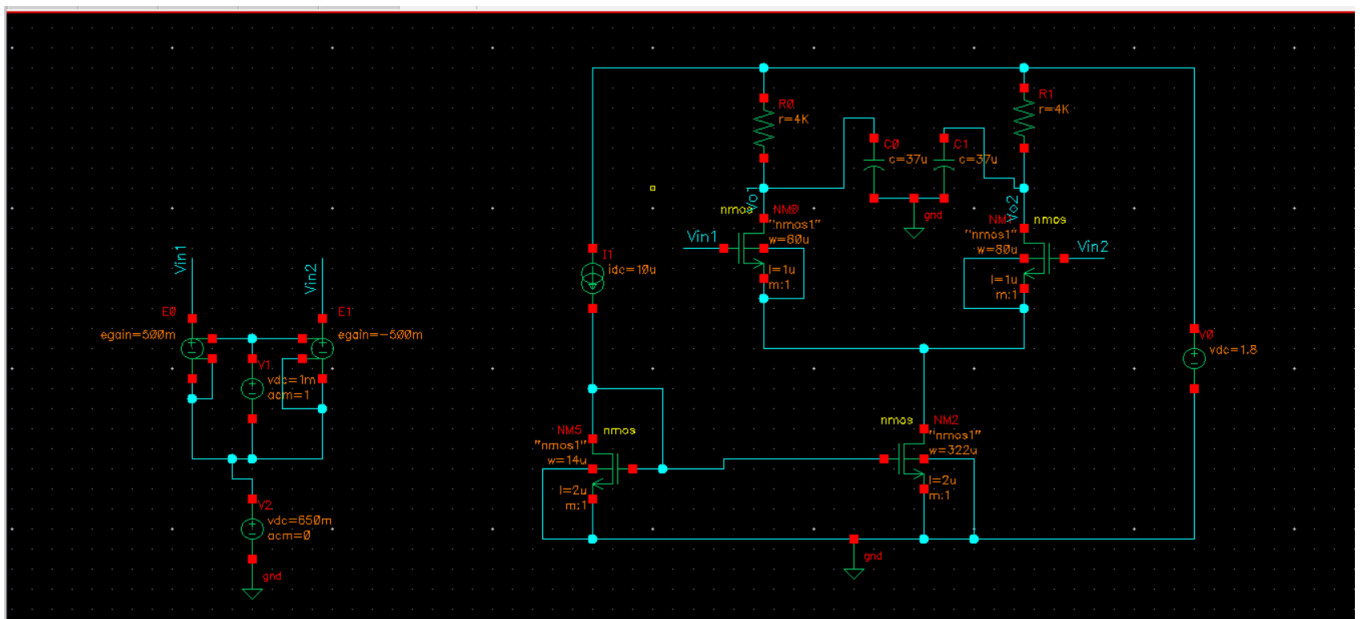


Figure 9: Circuit diagram for noise calculations

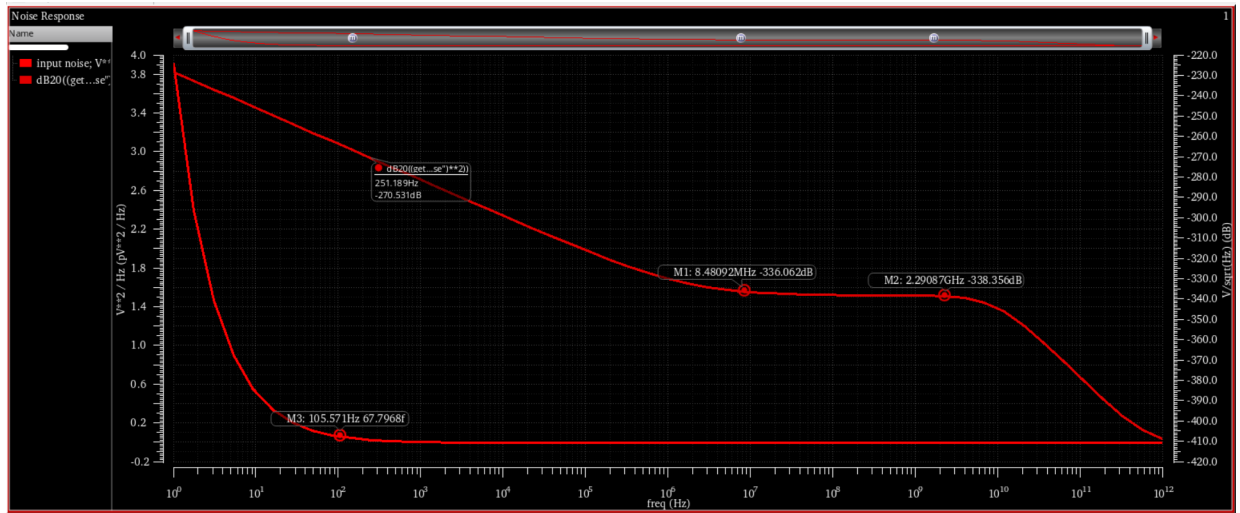


Figure 10: Input noise plot in dB and magnitude

Device	Param	Noise Contribution	% Of Total
/NM0	fn	1.9657e-16	50.03
/NM1	fn	1.95396e-16	49.73
/NM1	id	3.74458e-19	0.10

Integrated Noise Summary (in V^2) Sorted By Noise Contributors  
Total Summarized Noise = 3.92922e-16  
Total Input Referred Noise = 5.7701e-11  
The above noise summary info is for noise data

Figure 11: Noise summary

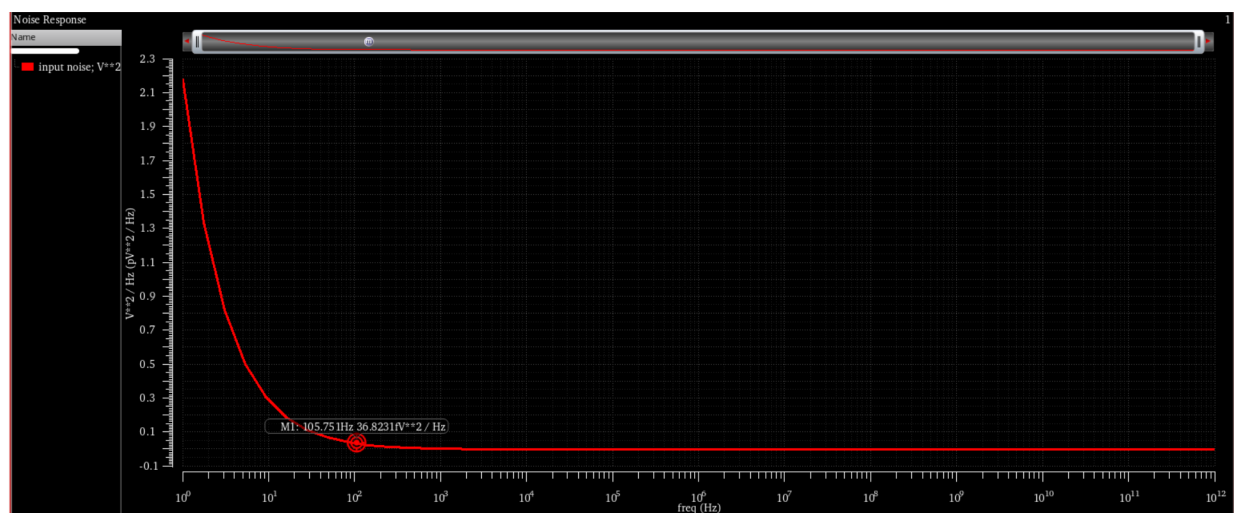


Figure 12: Input noise plot previous case

Device	Param	Noise Contribution	% Of Total
/NM0	id	7.73733e-07	44.07
/NM1	id	7.59546e-07	43.27
/R0	rn	1.04638e-07	5.96
/R1	rn	1.03792e-07	5.91
/NM0	fn	6.75705e-09	0.38

Integrated Noise Summary (in V^2) Sorted By Noise Contributors  
Total Summarized Noise = 1.7555e-06  
Total Input Referred Noise = 2.7529e-08  
The above noise summary info is for noise data

Device	Param	Noise Contribution	% Of Total
/NM0	id	7.73733e-07	44.07
/NM1	id	7.59546e-07	43.27
/R0	rn	1.04638e-07	5.96
/R1	rn	1.03792e-07	5.91
/NM0	fn	6.75705e-09	0.38

Integrated Noise Summary (in V^2) Sorted By Noise Contributors  
Total Summarized Noise = 1.7555e-06  
Total Input Referred Noise = 2.7529e-08  
The above noise summary info is for noise data

Figure 13: Noise summary for previous case

It is observed that when current increase noise decreases as current in previous case was  $10\mu\text{A}$  and in this case it is  $230\mu\text{A}$  and the input referred noise is  $5.7701\text{e-}11$  and  $2.7529\text{e-}8$  respectively.

The effect of power on PSD. The 3-dB reduction in noise occurs at a cost of doubling the power consumption, which is called "Linear Scaling". We can also say that the widths of the transistors and the resistor are doubled.

## 2 Design of differential amplifier with current mirror load

Design a differential amplifier with current mirror load, tail current source of  $23 \times (10) \mu\text{A}$ . The ICMR should be  $0.8\text{ V}$ ,  $\text{fugb,db} < 40\text{MHz}$  and maximize the voltage gain and minimize the common mode gain. The  $g_m/I_d$  ratio of input transistors should be less than 10. Bias the tail current source by using the available reference current of  $I_{\text{REF}} = 10 \mu\text{A}$ .

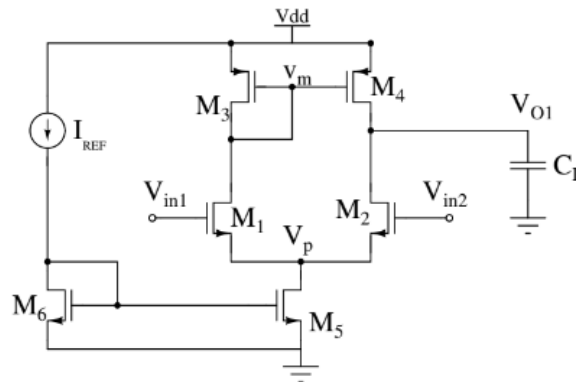


Figure 14: Differential amplifier with current mirror load

### 2.1 Hand calculations

Given  $g_m/I_d < 10$ , for input transistors,  $\text{ICMR} = 0.8\text{V}$ ,  $\text{fugb} < 40\text{MHz}$ ,  $I_{\text{ref}} = 10\mu\text{A}$  The tail current source  $= 230\mu\text{A}$  First we can calculate the ratio of  $W/L$  ratio of  $M3$  and  $M4$  which can be easily calculated to be equal to 23.



### 2.1.1 Calculating W/L for M3 and M4

For M3 transistor the value of W/L is calculated as follows;

$$I_d = 230\mu A$$

$$I_d = \frac{\mu C_{ox} W (V_{gs} - V_t)^2}{2L} \quad (10)$$

Taking the  $V_{gs} - V_t$  for M3 = 100mV we can find  $W/L = 153.32$ . the value of the W/L of M4 can be calculated by dividing the above by 23 which comes out to be 6.665.

### 2.1.2 Calculating the values of W/L of input Transistors

Here also the current can be said to be divisible by 2 because of the symmetry of the transistors.  $g_m/I_d < 10$  for input transistors

$$\frac{2I_d}{I_d(V_{gs1} - V_t)} < 10 \quad (11)$$

or  $V_{gs1} - V_t > 200\text{mV}$  or  $V_{gs1} > 700\text{mV}$  Also from these analysis we can say that  $g_m < 2.3\text{mS}$

From (7)

$$115\mu = 300\mu(.04)W/L*0.5 \text{ or } W/L = 19.16.$$

For the pmos transistors the value of W/L. similarly we can say

$$115\mu = 150\mu(0.01)(W/L)*0.5 \text{ or } W/L = 153.32$$

### 2.1.3 Calculating Cl

$f_{ugb} < 40\text{MHz}$  or

$$\frac{g_m}{2\pi C_l} < 40\text{MHz} \quad (12)$$

Put  $g_m = 2.3\text{mS}$  and calculating we get  $C_l > 9.15\text{pF}$

### 2.1.4 Calculating Vin,cm

$$V_{in,cm} = V_{gs1} + V_{gs3} - V_{th3} \quad V_{in,cm} > 700 + 100 = 800\text{mV}$$

**2.2 Show the plots verifying obtained swing, ICMR, differential gain and common mode gain.**

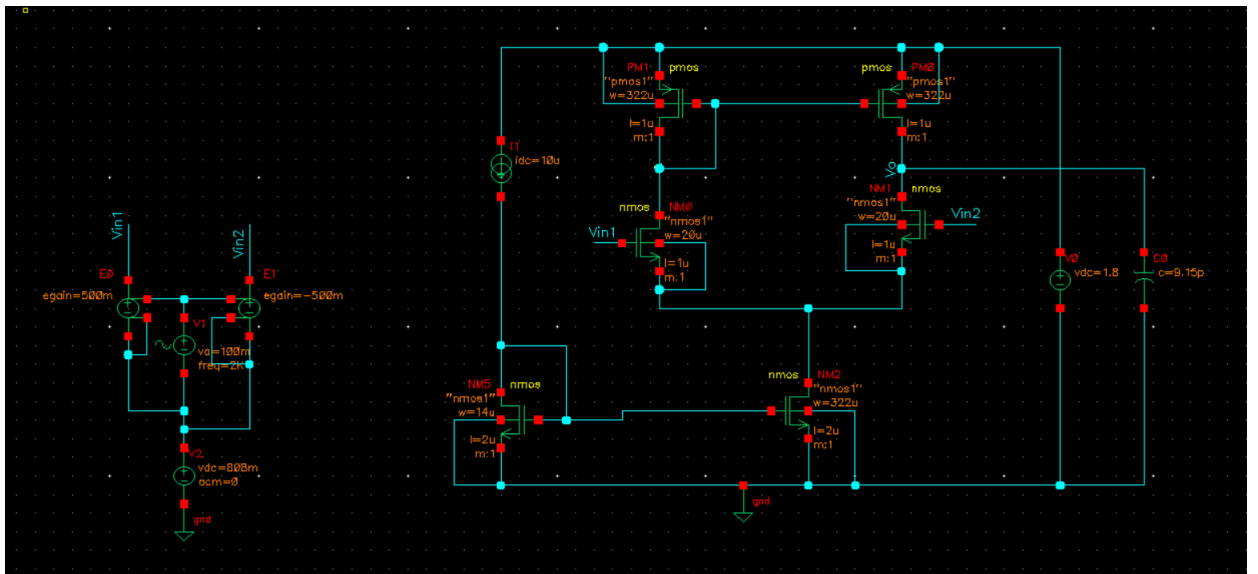


Figure 15: Ckt for ICMR calculations

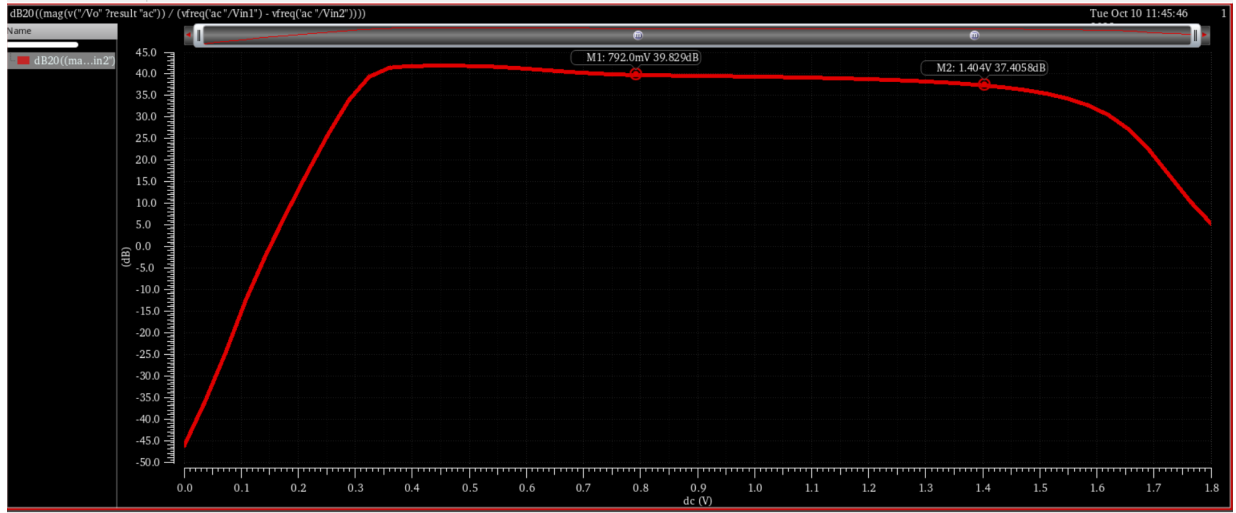


Figure 16: ICMR plot

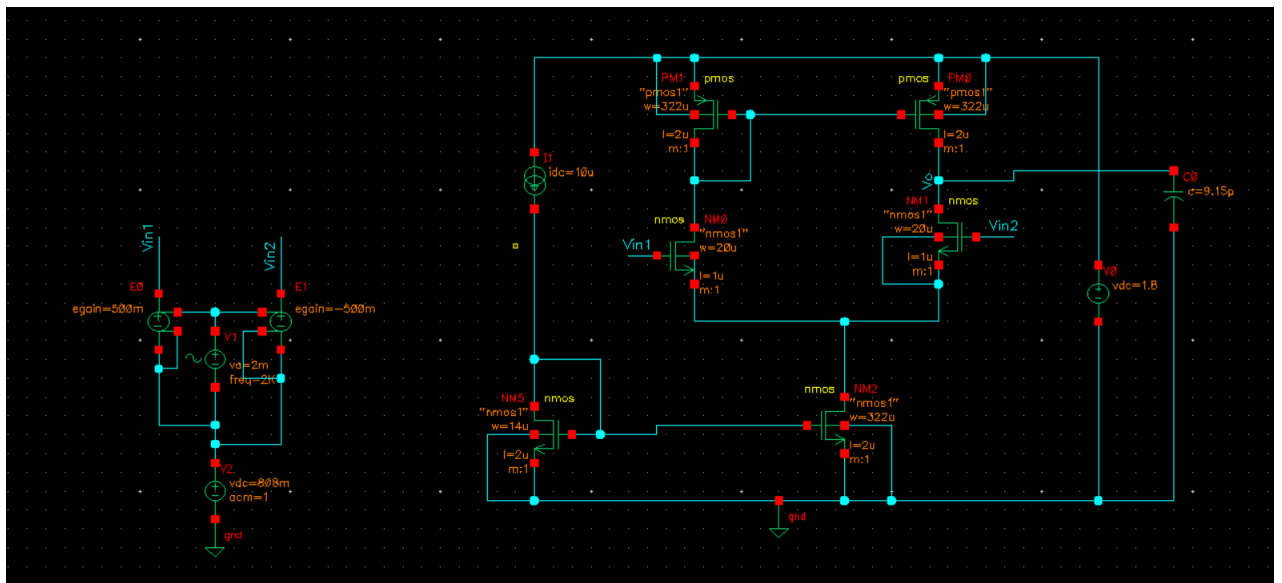


Figure 17: Ckt diagram for calculating different swings

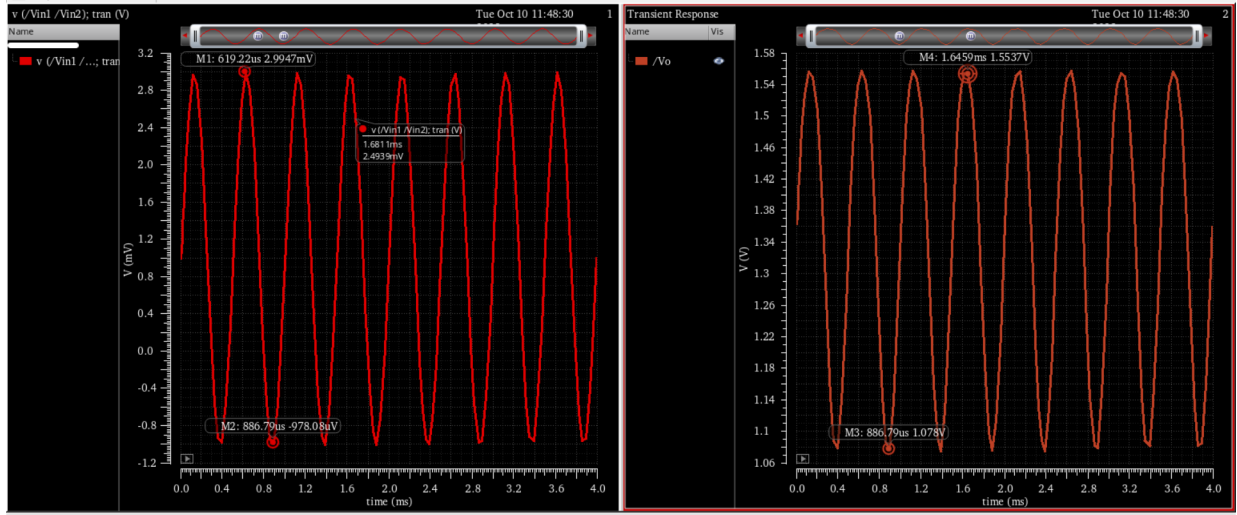


Figure 18: Transient response of the circuit

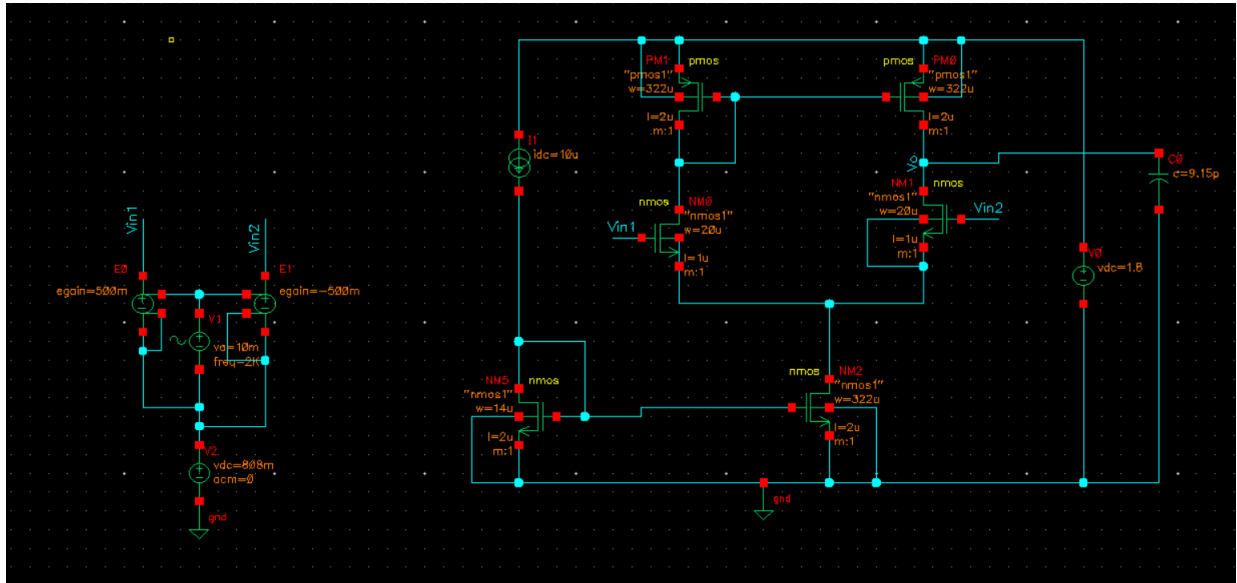


Figure 19: Ckt diagram for frequency analysis of Avdm

$$Avdm = g_{m1}(r_{o1} || r_{o4}) * \frac{2g_{m4}r_{o4} + 1}{2(g_{m4}r_{o4} + 1)} \quad (13)$$

$$\begin{aligned} g_{m1} &= 1.09 \text{ m} \\ r_{o1} &= 257.377 \text{ k}\Omega \\ g_{m4} &= 1.32 \text{ mS} \\ r_{o4} &= 226 \text{ k}\Omega \end{aligned}$$

$$Avdm = 1.09 \text{ m} * (257.377 \text{ K}\Omega || 226 \text{ K}\Omega) * \frac{2 * 1.32 \text{ m} * 226 \text{ K}\Omega + 1}{2(1.32 \text{ m} * 226 \text{ K}\Omega + 1)} \quad (14)$$

$$\begin{aligned} Avdm(\text{in dB}) &= 20\log(Avdm) = 42 \text{ dB} \\ f_{\text{ugb}} &< 40 \text{ MHz} \end{aligned}$$

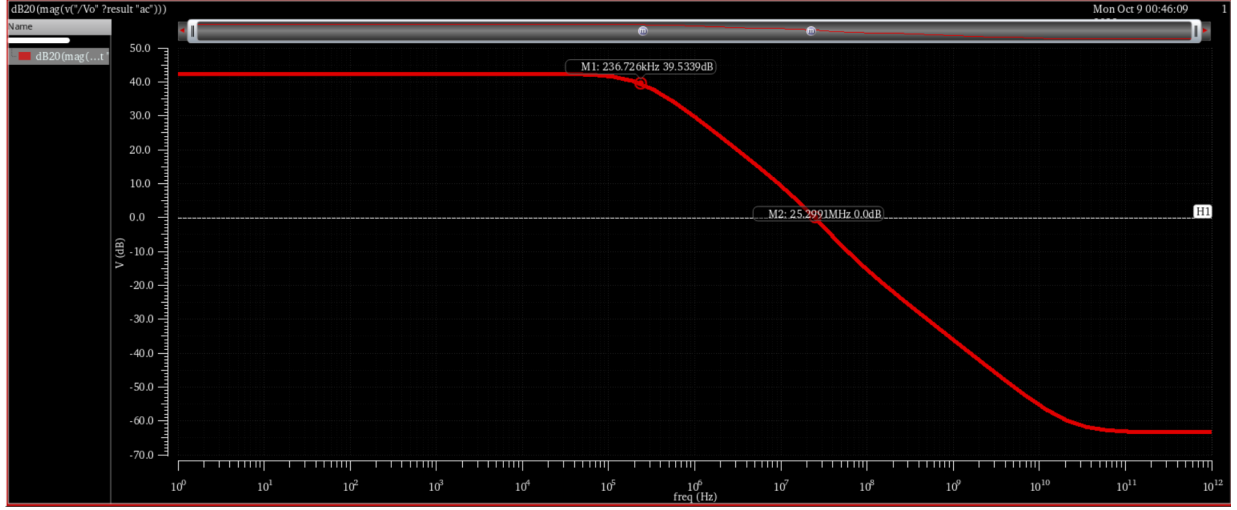


Figure 20: Differential gain wrt frequency

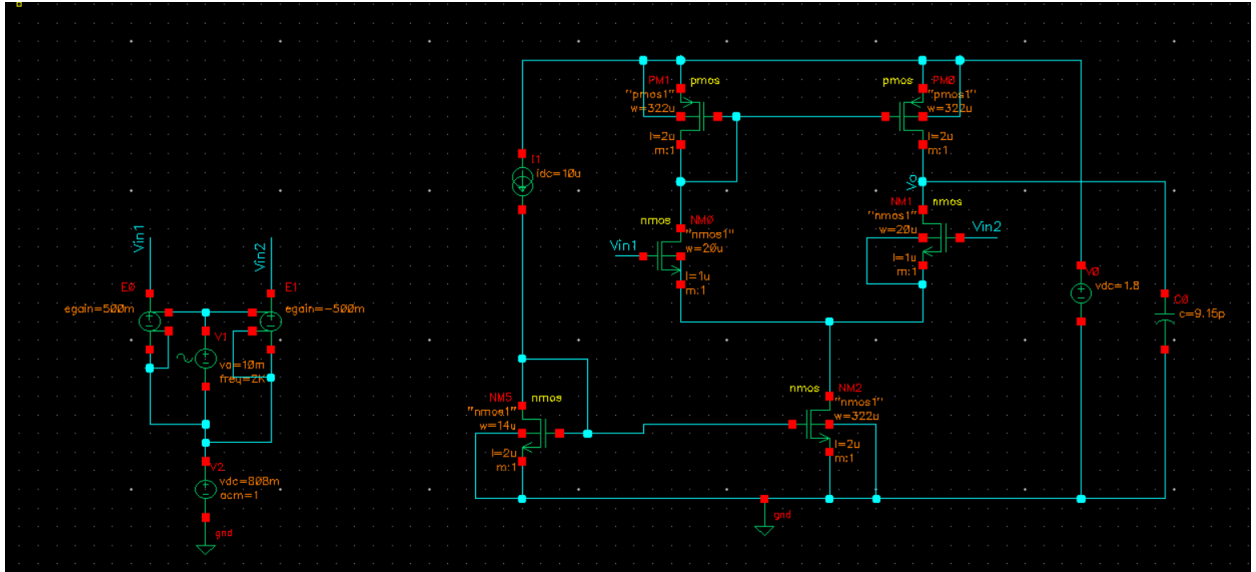


Figure 21: Ckt diagram for frequency relationship of  $A_{vcm}$

$$A_{vcm} = -\frac{1}{1 + 2g_{m1}R_{ss}} \frac{g_{m1}}{g_{m3}} \quad (15)$$

$$|A_{vcm}| = \frac{1}{1 + 2 * 1.09m * 7k} \frac{1.09m}{1.33m} = 0.0504 \quad (16)$$

$$|A_{vcm,cm}|_{dB} = 20\log(0.0504) = -25dB \quad (17)$$

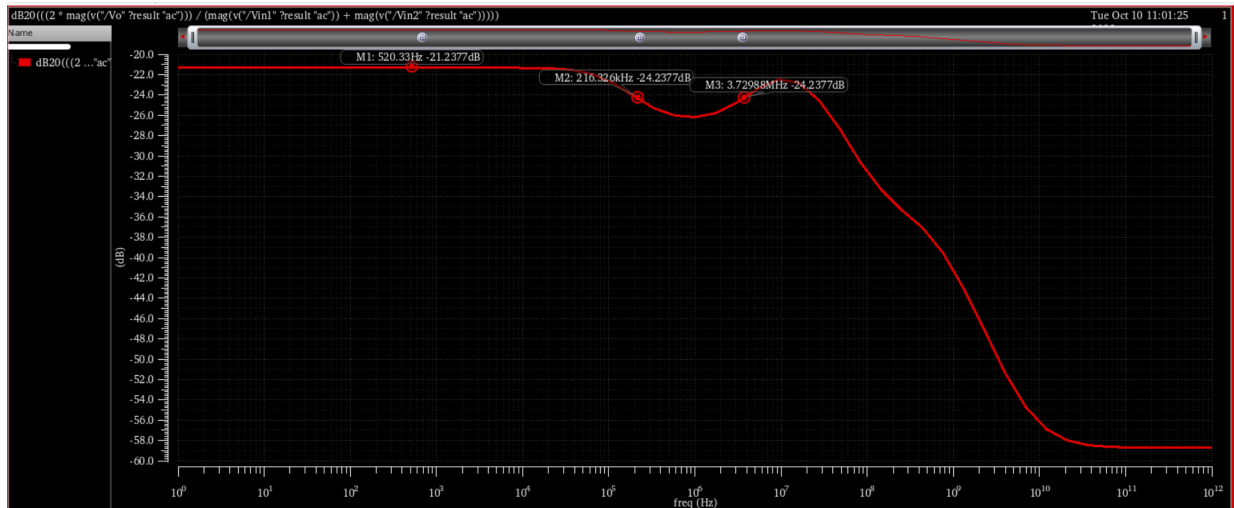


Figure 22: AvcM plot wrt frequency

2.3 What is the step input voltage at which this amplifier connected as a unity gain voltage buffer starts to slew?

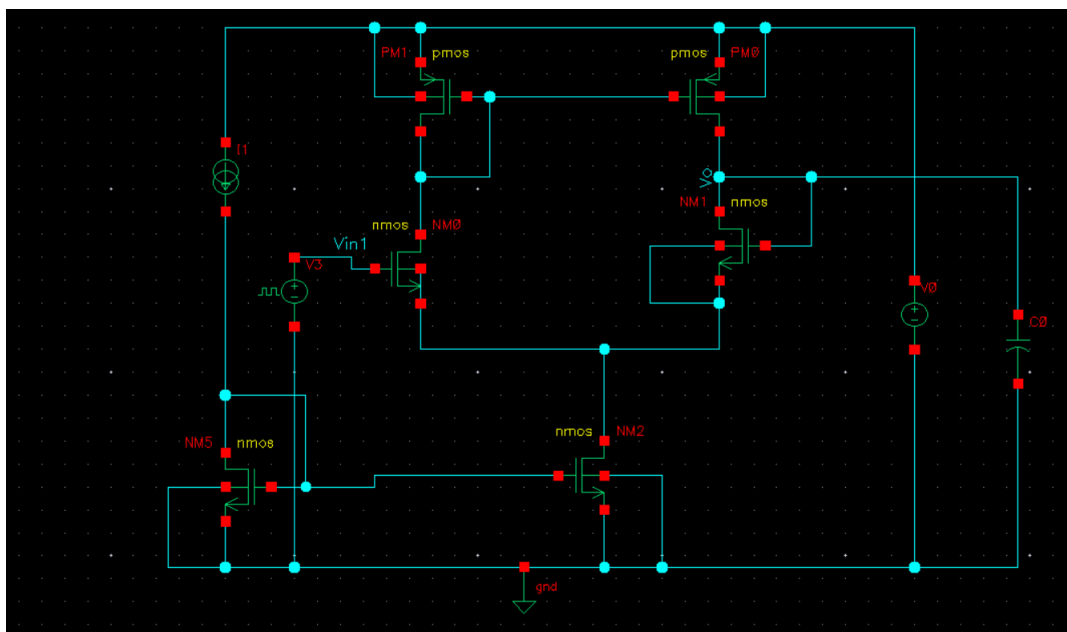


Figure 23: Ckt for slew rate

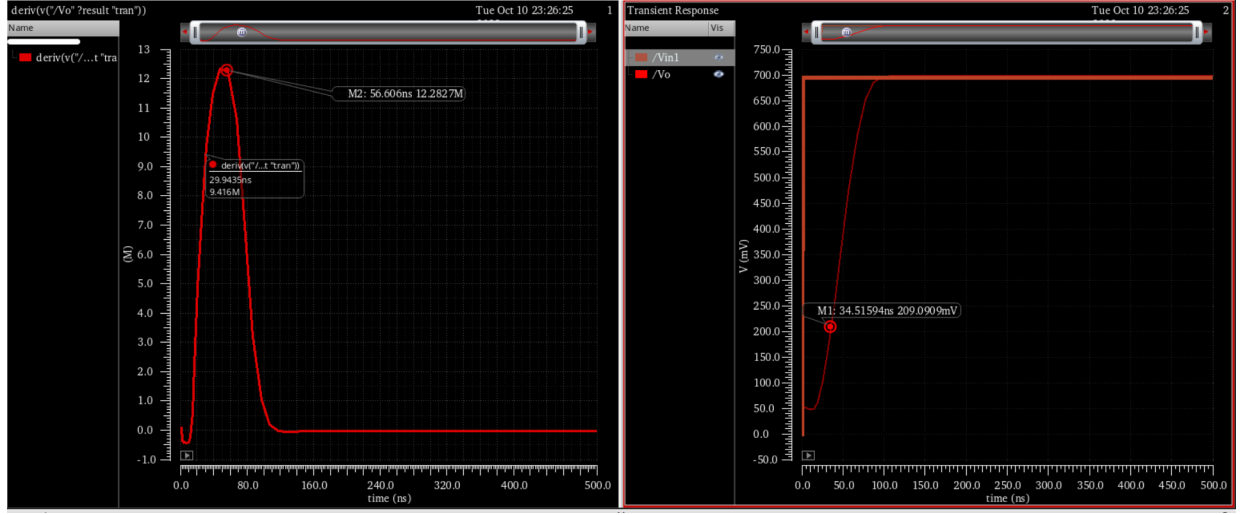


Figure 24: Plot observed

Calculations Slew rate

$$V_o = V_{max} \left( \exp\left(\frac{-t}{\tau}\right) - 1 \right) \quad (18)$$

$$\frac{dV_o}{dt} = \frac{V_{max}}{\tau} \quad (19)$$

For slewing

$$\frac{I_o}{C_l} < \frac{V_{max}}{\tau} \quad (20)$$

$$\tau = C_l / g_m \quad (21)$$

or

$$I_o / C_l < V_{max} * g_m / C_l \quad (22)$$

or

$$V_{max} > \frac{V_o}{g_m} \quad (23)$$

$$I_o = \text{Tail current Source} = 230 \mu A \quad g_{m2} = 1.10 \text{ mS}$$

$$\tau = \frac{C_L}{g_{m2}} \quad (24)$$

$$\tau = \frac{9.15 \text{ pF}}{1.10 \text{ m}} = 8.318 \text{ nSec} \quad (25)$$

$$\frac{I_o}{C_L} < \frac{V_{max}}{C_L} * g_{m2} \quad (26)$$

$$V_{max} > \frac{I_o}{g_{m2}} \quad (27)$$

$$V_{max} > \frac{230 \mu A}{1.10 \text{ m}} \quad (28)$$

$$V_{max} > 209.0909 \text{ mV} \quad (29)$$

2.4 Calculate the output pole, mirror pole and mirror zero. Compare the calculated and simulated values using pz analysis.

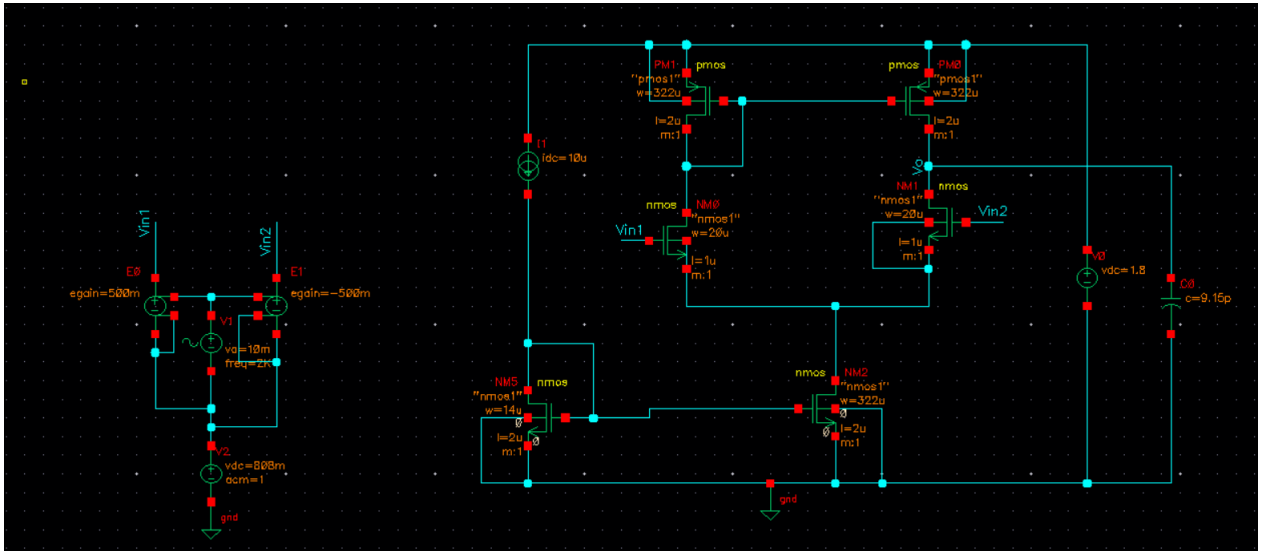


Figure 25: Ckt for pz analysis

	Real	Imaginary	Qfactor
1	-1.34338e+05	0.00000e+00	5.00000e-01
2	-2.38288e+07	0.00000e+00	5.00000e-01

Zeros (Hz) at V( <u>Vo,net011</u> )/V1			
	Real	Imaginary	Qfactor
1	-2.32302e+07	0.00000e+00	5.00000e-01
2	2.31908e+10	0.00000e+00	-5.00000e-01

Constant factor = 7.96969e-04

Figure 26: Pole Zero outputs